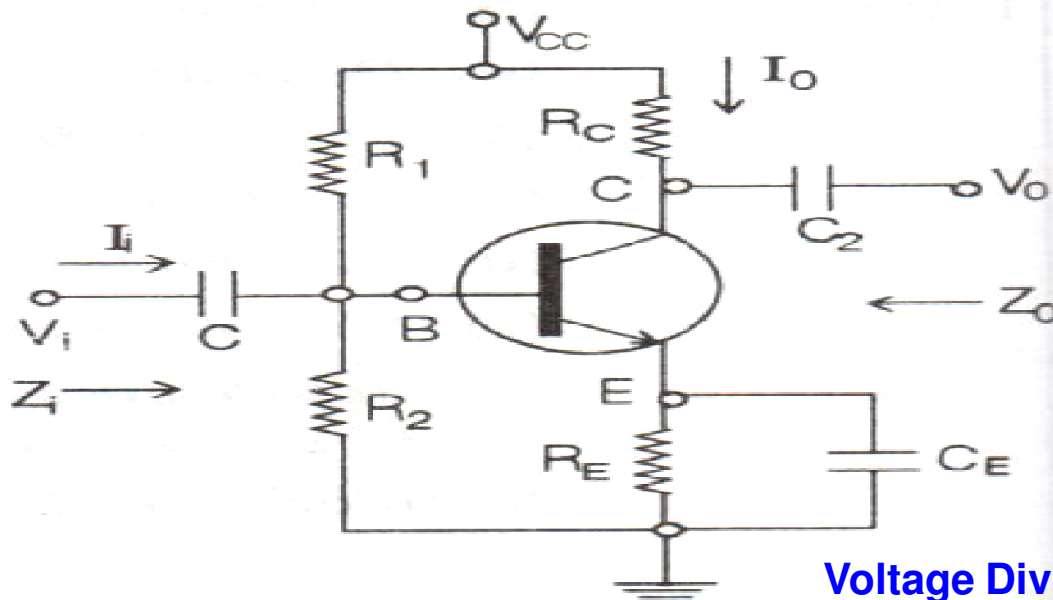


Small Signal Analysis of BJTs Single Stage Amplifier


Voltage Divider Circuit



Voltage-divider bias is the most widely used type of bias circuit. Only one power supply is needed and voltage-divider bias is more stable (β independent) than other bias types. For this reason it will be the primary focus for study.

Voltage Divider Bias Configuration

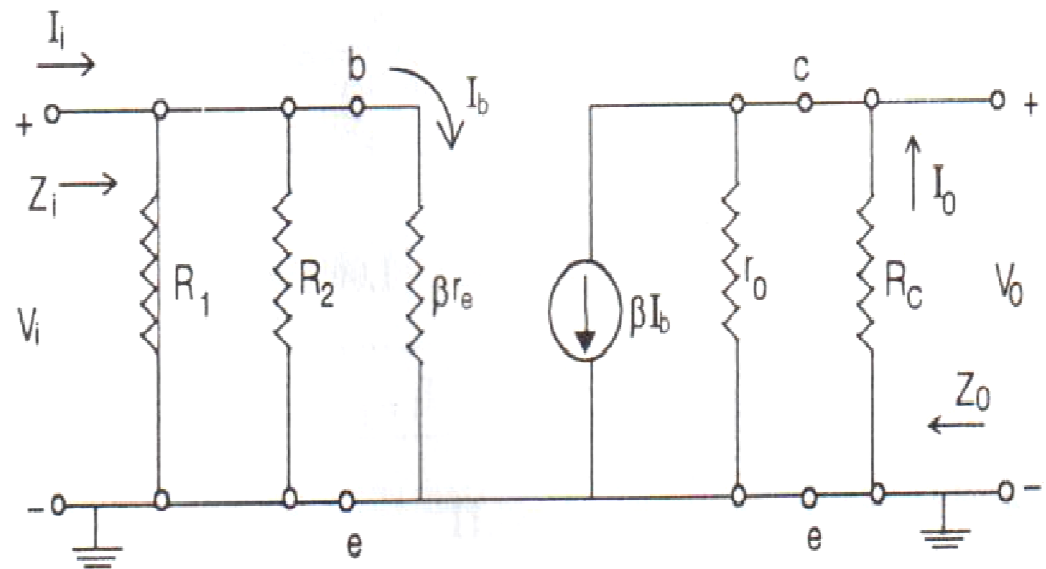Note the absence of R_E due to the low impedance shorting effect of the bypass capacitor, C_E . That is at the frequency of operation, the reactance of the capacitor is so small compared to R_E that it is treated as short circuit across R_E .



AC Equivalent Circuit Configuration

Parallel combination of resistor

$$R' = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2} \quad (1)$$

Input Impedance

Z_i : From Fig.

$$Z_i = R' \parallel \beta r_e \quad (2)$$

Output Impedance

Z_o : From Fig. with V_i set to 0 V resulting in $I_b = 0 \mu A$ and $\beta I_b = 0 \text{ mA}$

$$Z_o = R_C \parallel r_o \quad (3)$$

If $r_o \geq 10R_C$.

$$Z_o \cong R_C \quad r_o \geq 10R_C \quad (4)$$

Voltage gain

A_v : Since R_C and r_o are in parallel

$$V_o = -(\beta I_b)(R_C \parallel r_o) \quad (5)$$

$$I_b = \frac{V_i}{\beta r_e}$$

$$V_o = \beta \left(\frac{V_i}{\beta r_e} \right) (R_C \parallel r_o) \quad (6)$$

From Eq: (5) and (6)

$$A_v = \frac{V_o}{V_i} = - \frac{R_C \parallel r_o}{r_e} \quad A_v = \frac{V_o}{V_i} \cong - \frac{R_C}{r_e} \quad r_o \geq 10R_C \quad (7)$$

Current gain

Here: $R' = R_1 \parallel R_2 = R_B$

For $r_o \geq 10R_C$

$$A_i = \frac{I_o}{I_i} = \frac{\beta R' r_o}{(r_o + R_C)(R' + \beta r_e)} \quad (8)$$

$$A_i = \frac{I_o}{I_i} \cong \frac{\beta R' r_o}{r_o (R' + \beta r_e)} \quad (9)$$

and

$$A_i = \frac{I_o}{I_i} \cong \frac{\beta R'}{R' + \beta r_e} \quad r_o \geq 10R_C \quad (10)$$

And if $R' \geq 10\beta r_e$,

$$A_i = \frac{I_o}{I_i} = \frac{\beta R'}{R'}$$

and

$$A_i = \frac{I_o}{I_i} \cong \beta \quad r_o \geq 10R_C, R' \geq 10\beta r_e \quad (11)$$

As an option,


$$A_i = -A_v \frac{Z_i}{R_C} \quad (12)$$

EMITTER FOLLOWER CONFIGURATION


- Emitter follower is a **common collector** transistor configuration.
(When output taken from the emitter terminal of the transistor is known as emitter follower)
- Emitter follower can be designed by simply **short circuit RC** and **remove bypass capacitor** in RC coupled amplifier.
- Emitter follower gives **high input impedance** and **low output impedance**.
- Emitter follower can be used as **buffer**.
- Emitter follower is also known as **voltage follower**.
- The emitter follower configuration frequently used for **impedance matching**

Emitter Follower Configuration

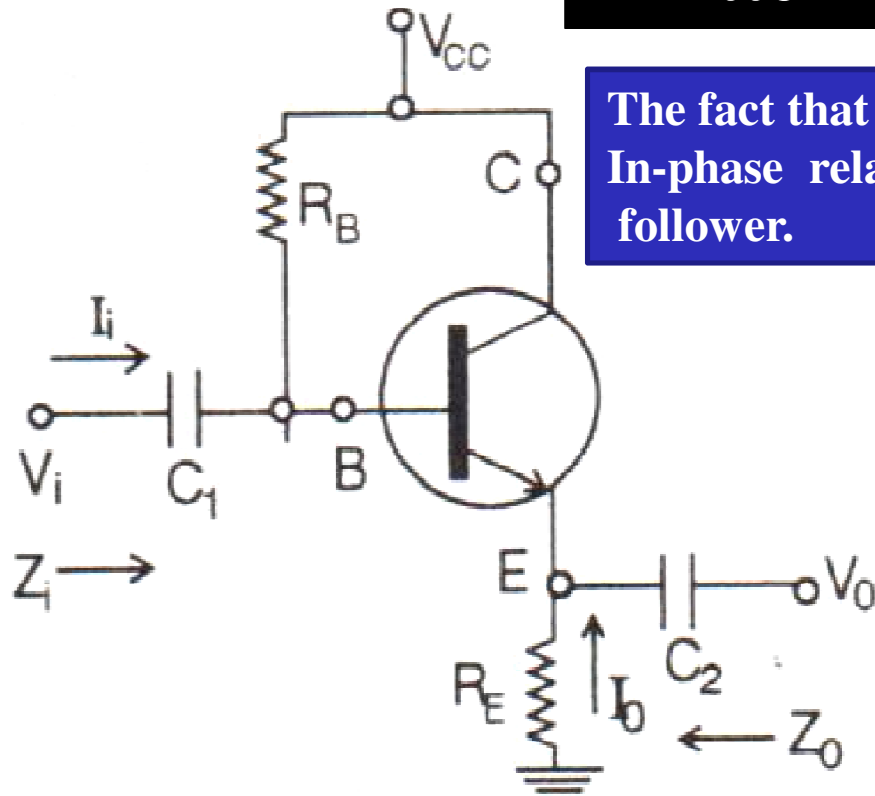The fact that V_o “follows” the magnitude of V_i with an In-phase relationship accounts for the terminology emitter follower.



Emitter Follower Configuration

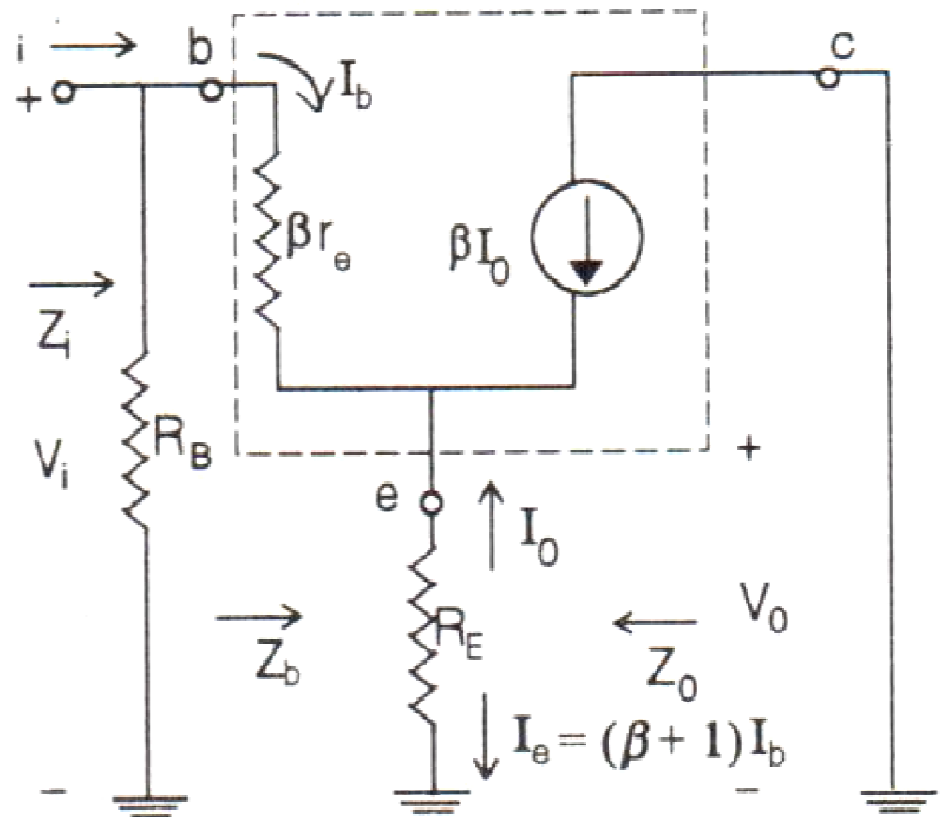

Ro Equivalent Circuit for AC Equivalent Network

Input Impedance:

Z_i : The input impedance is determined in the same manner as described

$$Z_i = R_B \parallel Z_b \quad (1)$$

with

$$Z_b = \beta r_e + (\beta + 1)R_E \quad (2)$$

or

$$Z_b \cong \beta(r_e + R_E)$$

and

$$Z_b \cong \beta R_E \quad (3)$$

Output Impedance:

Z_o : The output impedance is best described by first writing the equation for the current I_b :

$$I_b = \frac{V_i}{Z_b} \quad (4)$$

and then multiplying by $(\beta + 1)$ to establish I_e . That is,

$$I_e = (\beta + 1)I_b = (\beta + 1) \frac{V_i}{Z_b} \quad (5)$$

Substituting for Z_b gives

$$I_e = \frac{(\beta + 1)V_i}{\beta r_e + (\beta + 1)R_E} \quad (6)$$

or

$$I_e = \frac{V_i}{[\beta r_e / (\beta + 1)] + R_E} \quad (7)$$

but

$$(\beta + 1) \cong \beta$$


and

$$\frac{\beta r_e}{\beta + 1} \cong \frac{\beta r_e}{\beta} = r_e$$

so that

$$I_e \cong \frac{V_i}{r_e + R_E}$$

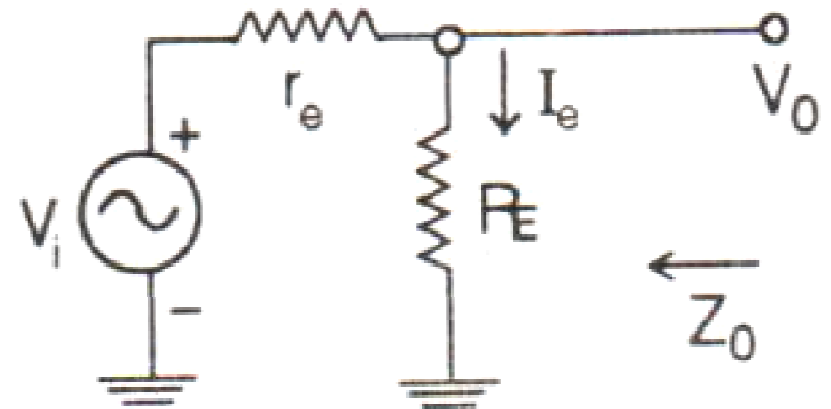If we now construct the network defined by Eq.



To determine Z_o , V_i is set to zero and

$$Z_o = R_E \parallel r_e$$

(8)

Since R_E is typically much greater than r_e the following approximation is often applied :

$$Z \cong r_e$$

(9)

Voltage gain

A_v : Figure can be utilized to determine the voltage gain through an application of the voltage-divider rule :

$$V_o = \frac{R_E V_i}{R_E + r_e}$$

and

$$A_v = \frac{V_o}{V_i} = \frac{R_E}{R_E + r_e} \quad (9)$$

Since R_E is usually much greater than r_e , $R_E + r_e \cong R_E$ and

$$A_v = \frac{V_o}{V_i} \cong 1$$

Current gain

A_i : From Fig. ,

$$I_b = \frac{R_B I_i}{R_B + Z_b} \quad \text{or} \quad \frac{I_b}{I_i} = \frac{R_B}{R_B + Z_b}$$

and

$$I_o = -I_e = -(\beta + 1)I_b \quad \text{or} \quad \frac{I_o}{I_b} = -(\beta + 1)$$

so that

$$A_i = \frac{I_o}{I_i} = \frac{I_o}{I_b} \frac{I_b}{I_i} = -(\beta + 1) \frac{R_B}{R_B + Z_b}$$

and since

$$(\beta + 1) \cong \beta,$$

$$A_i \cong \frac{\beta R_B}{R_B + Z_b} \quad (10)$$


or

$$A_i = -A_v \frac{Z_i}{R_E} \quad (11)$$


Common-Base (CB) Configuration

The input (V_i) is applied to the emitter and the output (V_o) is from the collector.

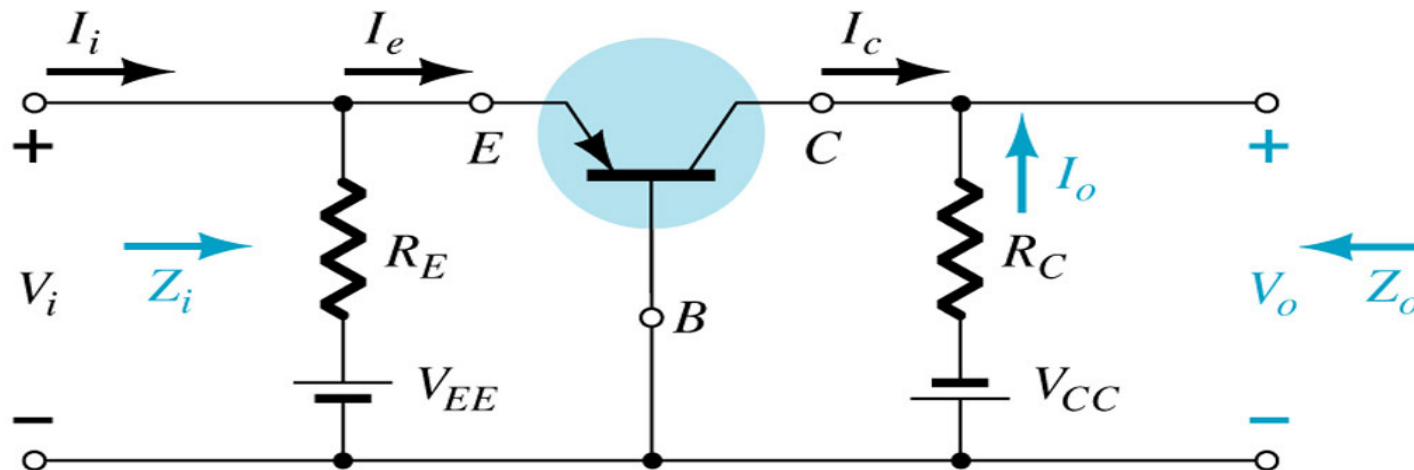
The Common-Base is characterized as having low input impedance and high output impedance with a current gain less than 1 and a very high voltage gain.



Common Base Configuration

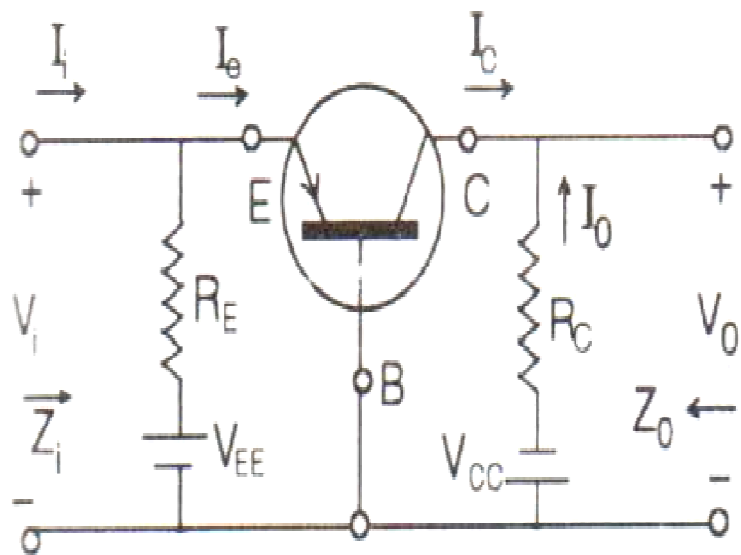

CB Configuration

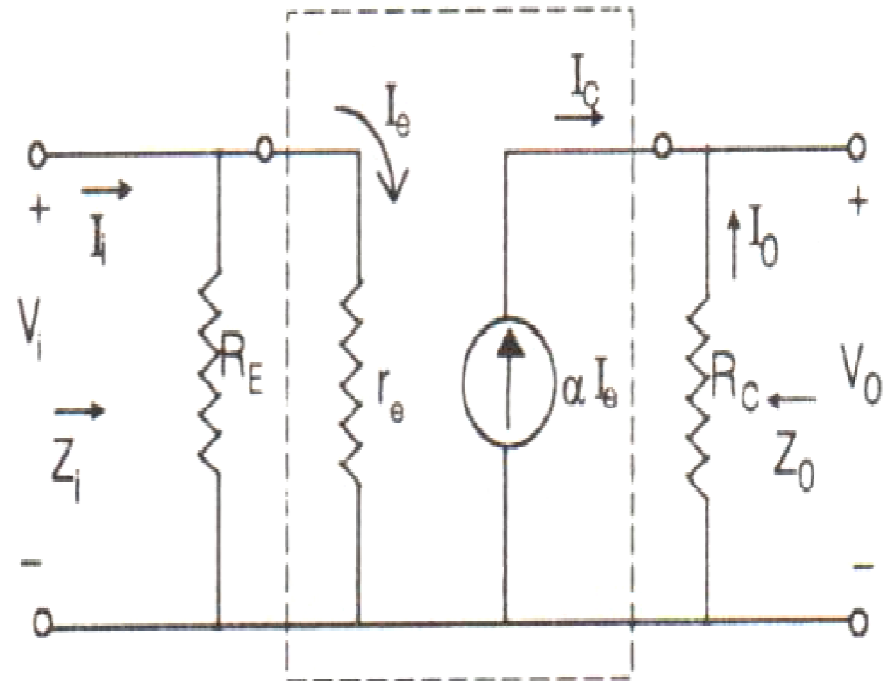

AC Equivalent Circuit

Input Impedance:

Output Impedance: $Z_i :$ $Z_i = R_E \parallel r_e$ (1)

$Z_o :$ $Z_o = R_C$ (2)

Voltage gain: $A_v :$

$$V_o = -I_o R_C = -(-I_c) R_C = \alpha I_e R_C \quad (3)$$

with $I_e = \frac{V_i}{r_e}$ (4)

so that $V_o = \alpha \left(\frac{V_i}{r_e} \right) R_C$ (5)

and $A_v = \frac{V_o}{V_i} = \frac{\alpha R_C}{r_e} \cong \frac{R_C}{r_e}$ (6)

Current gain: $A_i :$ Assuming that $R_E \gg r_e$ yields

$$I_e = I_i \quad (7)$$

and $I_o = -\alpha I_e = -\alpha I_i$

$$A_i = \frac{I_o}{I_i} = -\alpha \cong -1 \quad (8)$$

Phase Relationship

A CB amplifier configuration has no phase shift between input and output.

