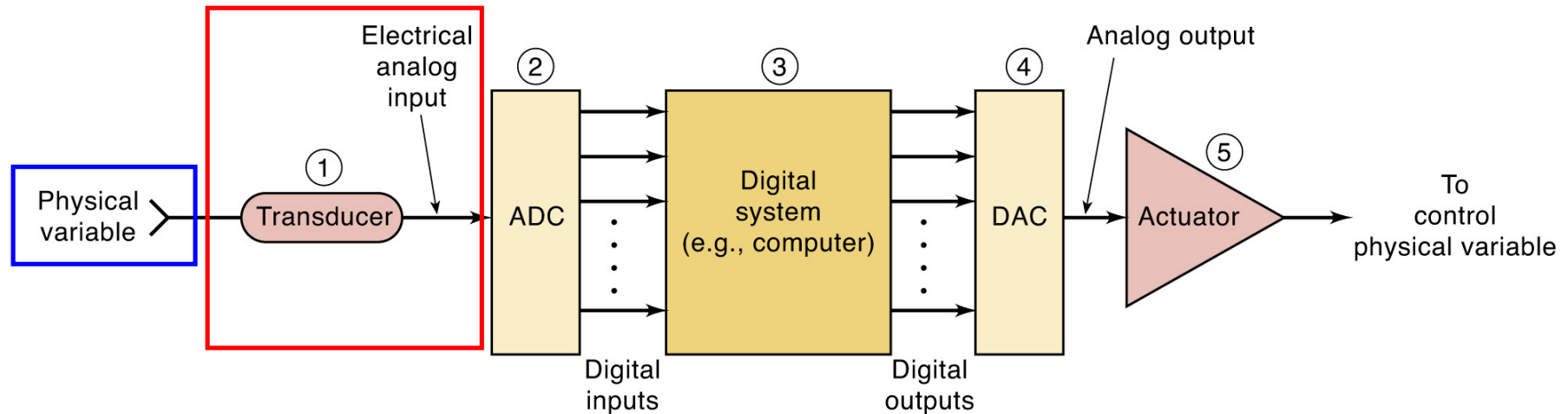



Interfacing With the Digital Analog World

Interfacing With the Analog World

- Most physical variables are analog, and can take on any value within a continuous range of values.
 - Normally a nonelectrical quantity.
- A **transducer** converts the physical variable to an electrical variable.
 - Thermistors, photo-cells, photodiodes, flow meters, pressure transducers, tachometers, etc.




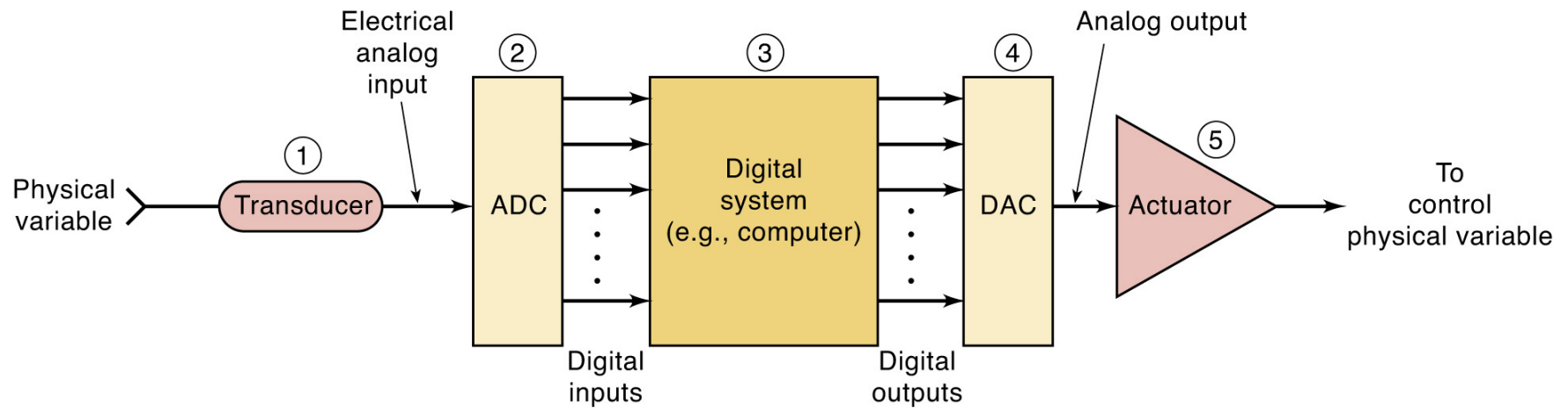- The transducer's electrical analog output is the analog input to the **analog-to-digital converter**.
- The ADC converts analog input to a digital output
 - Output consists of a number of bits that represent the value of the analog input.
 - The binary output from the ADC is proportional to the analog input voltage.




Digital output from the computer is connected to a **digital-to-analog converter (DAC)**.
 Converted to a proportional analog voltage/current.

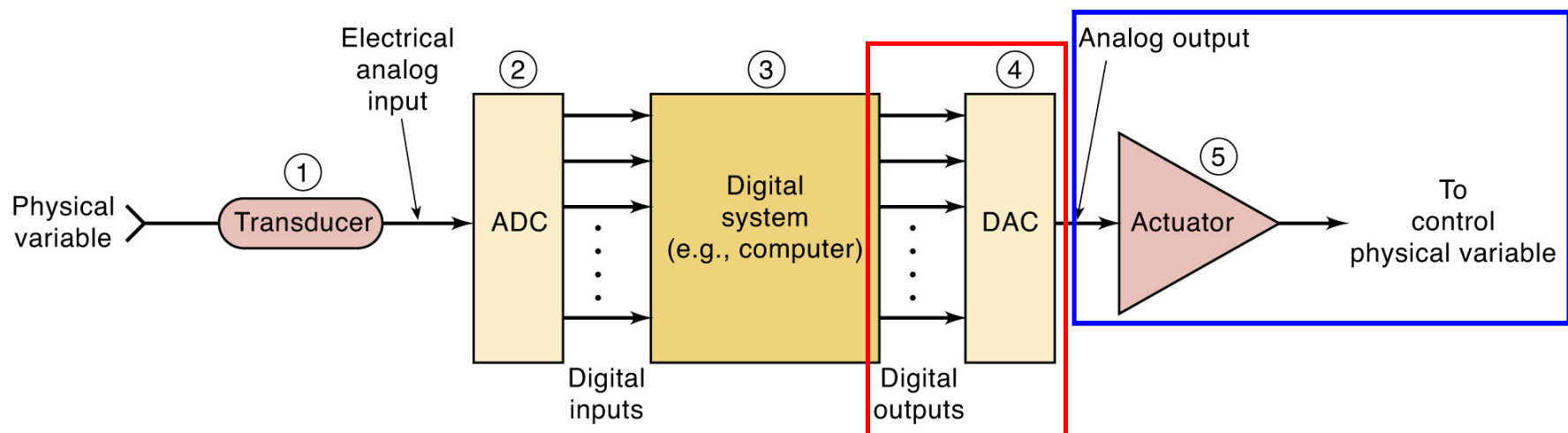- The analog signal is often connected to some device or circuit that serves as an actuator to control the physical variable.
 - An electrically controlled valve or thermostat, etc.



Digital to Analog Conversion

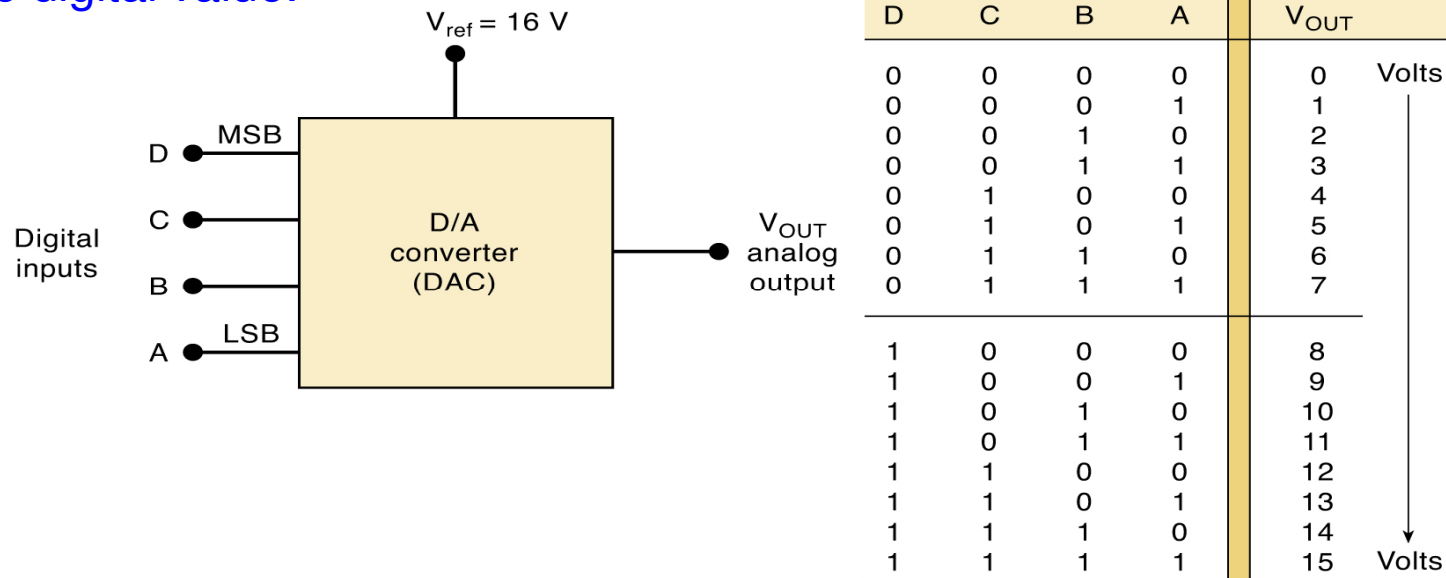- Many A/D conversion methods utilize the D/A conversion process.
- Converting a value represented in *digital* code to a voltage or current proportional to the digital value.



•For each input number, the D/A converter output voltage is a unique value—in general:

$$\text{analog output} = K \times \text{digital input}$$

...where K is the proportionality factor and is a constant value for a given DAC connected to a fixed reference voltage.

- The quantity of possible output values can be increased, and the difference between successive values decreased—by increasing the input bits.

Allowing output more & more like an analog quantity that varies continuously over a range of values.

A “pseudo-analog” quantity, which approximates pure analog, referred to as analog for convenience.

Each digital input contributes a different amount to the analog output—*weighted* according to their position in the binary number.

<i>D</i>	<i>C</i>	<i>B</i>	<i>A</i>		V_{OUT} (V)
0	0	0	1	→	1
0	0	1	0	→	2
0	1	0	0	→	4
1	0	0	0	→	8

Weights are successively doubled for each bit, beginning with the LSB.

V_{OUT} can be considered to be the weighted sum of the digital inputs.


D	C	B	A		V_{OUT}
0	0	0	0		0
0	0	0	1		1
0	0	1	0		2
0	0	1	1		3
0	1	0	0		4
0	1	0	1		5
0	1	1	0		6
0	1	1	1		7
1	0	0	0		8
1	0	0	1		9
1	0	1	0		10
1	0	1	1		11
1	1	0	0		12
1	1	0	1		13
1	1	1	0		14
1	1	1	1		15

Volts

Volts

- The **Resolution** of a D/A converter is defined as the smallest change that can occur in analog output as a result of a change in digital input.

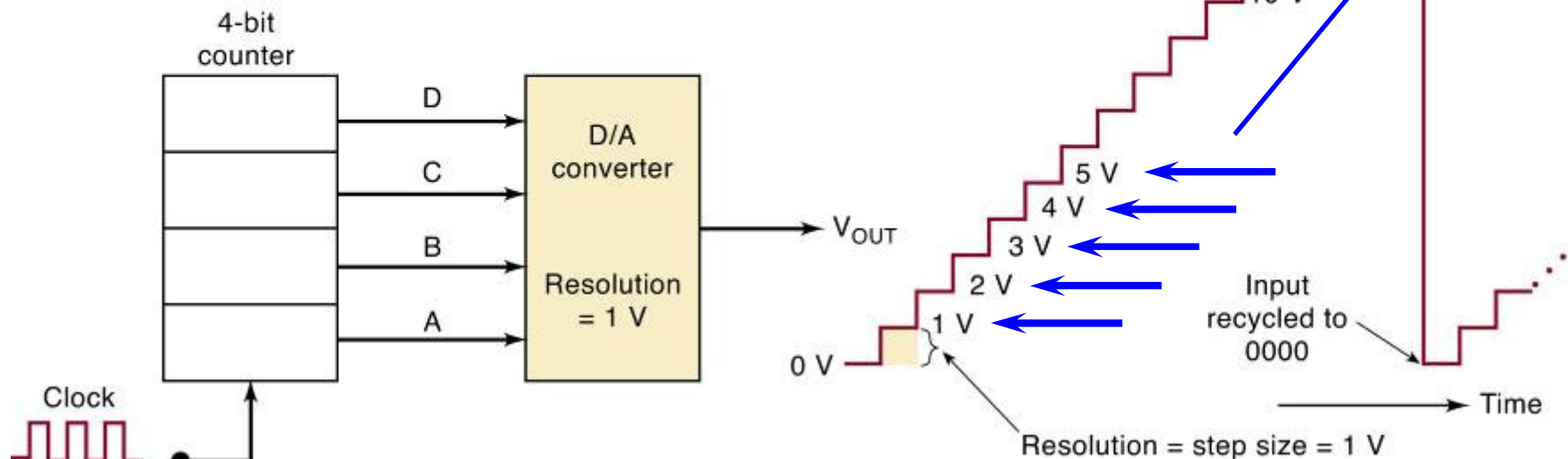Always equal to the weight of the LSB, called the **step size**, it is the amount V_{OUT} will change as digital input value changes from one step to the next.



- Resolution (step size) is the same as the DAC input/output proportionality factor:

$$\text{analog output} = K \times \text{digital input}$$

...where K is the proportionality factor and is a constant value for a given DAC connected to a fixed reference voltage.

Digital to Analog Conversion

- Many DACs can also produce negative voltages by making slight changes to the analog circuitry on the output of the DAC.

	Signed 2's Complement	DAC Inputs	DAC V_{out}
Most positive	01111111	11111111	$\sim + V_{ref}$
Zero	00000000	10000000	0 V
Most negative	10000000	00000000	$-V_{ref}$

Other DACs may have the extra circuitry built in and accept 2's complement signed numbers as inputs.


DAC Applications

- Used when a digital circuit output must provide an analog voltage or current.
 - **Control**—use a digital computer output to adjust motor speed or furnace temperature.
 - **Automatic testing**—computer generated signals to test analog circuitry.
 - **Signal reconstruction**—restoring an analog signal after it has been converted to digital.
 - **Digital amplitude control**—used to reduce the amplitude of an analog signal.
 - **Serial DACs**—with a built-in serial in/parallel out shift register—many have more than one DAC on the same chip.


Analog to digital Conversion

- An analog-to-digital converter takes an analog input voltage and, after a certain amount of time, produces a digital output code that represents the analog input.
 - Several important types of ADCs utilize a DAC as part of their circuitry.
- The Op amp comparator ADC
 - Variations differ in how the control section continually modifies numbers in the register

General diagram of one class of ADCs.

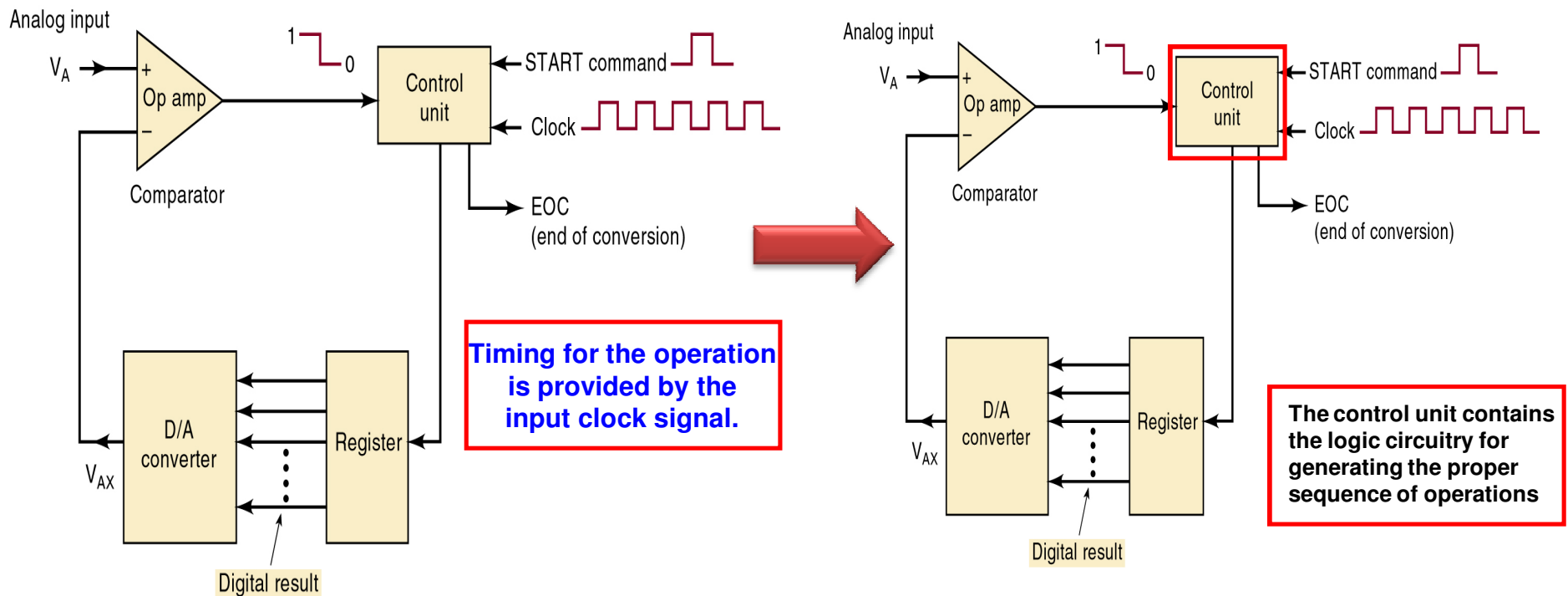

General diagram of one class of ADCs.

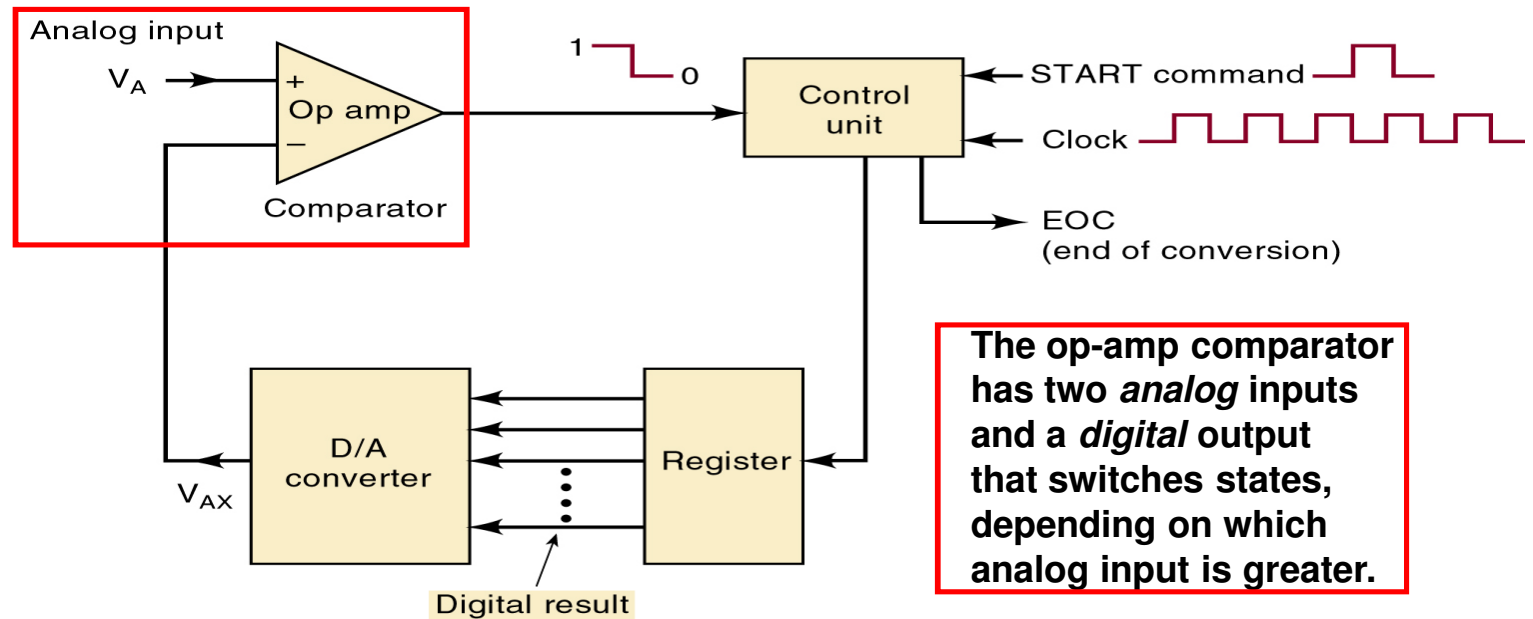


- **Basic operation of ADC types:**

- The START command pulse initiates the operation.
- At a rate determined by the clock, the control unit continually modifies the binary number in the register.
- The binary number in the register is converted to an analog voltage (V_{AX}), by the DAC.
- The comparator compares V_{AX} with analog input V_A .
 - While $V_{AX} < V_A$, comparator output stays HIGH.
 - When V_{AX} exceeds V_A by at least an amount equal to V_T (threshold voltage), comparator out-put goes LOW and stops modifying the register number.
- The control logic activates the end-of-conversion signal, *EOC*, when the conversion is complete.

- One of the simplest versions of the general ADC uses a binary counter as the register and allows the clock to increment the counter one step at a time until $V_{AX} > V_A$.
- Called a **digital-ramp ADC** because the waveform at V_{AX} is a step-by-step ramp.

A/D resolution and accuracy.

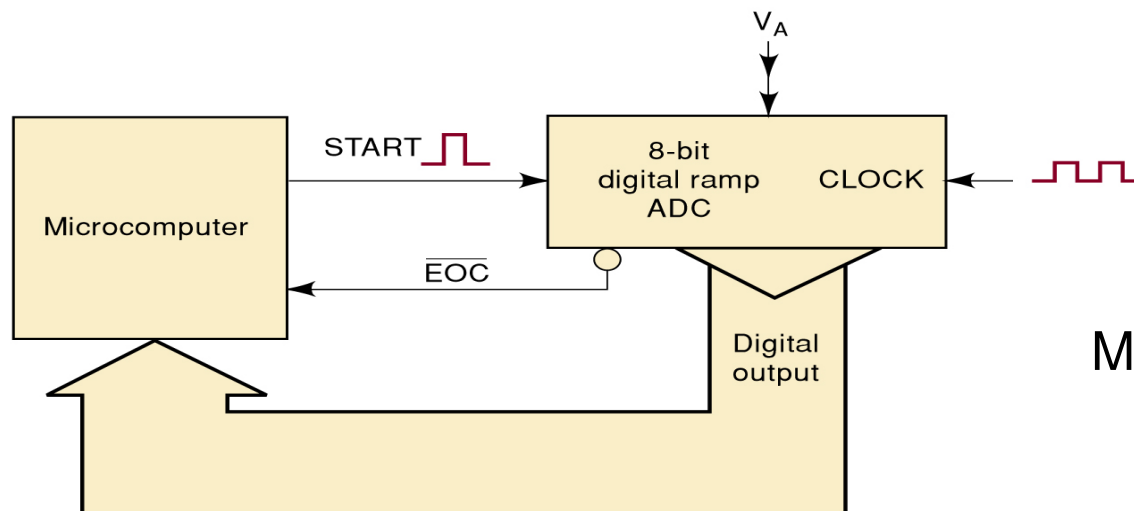- Measurement error is unavoidable.
- Reducing the step size can reduce but not eliminate potential error—called **quantization error**.
- **Data Acquisition:** The process by which the computer acquires digitized analog data is called *data acquisition*.
- Acquiring a single data point's value is referred to as **sampling** the analog signal. That data point is often called a *sample*




Microcomputer connected to a digital-ramp ADC for data acquisition.

Typical ADC Architecture for Applications

- **Most ADC applications fall into one of four areas:**
 - Precision industrial measurement.
 - Voice/audio.
 - Data acquisition.
 - High speed.
- Analog voltage connected directly to an ADC input conversion can be adversely affected if analog voltage is changing during the conversion time.
- Stability of conversion can be improved by using a **sample-and-hold (S/H) circuit**.
 - To hold the analog voltage constant while the A/D conversion is taking place.
- In a computer-controlled data acquisition system the sample-and-hold switch would be controlled by a digital signal from the computer.
 - The amount of time the switch would have to remain closed is called the **acquisition time**

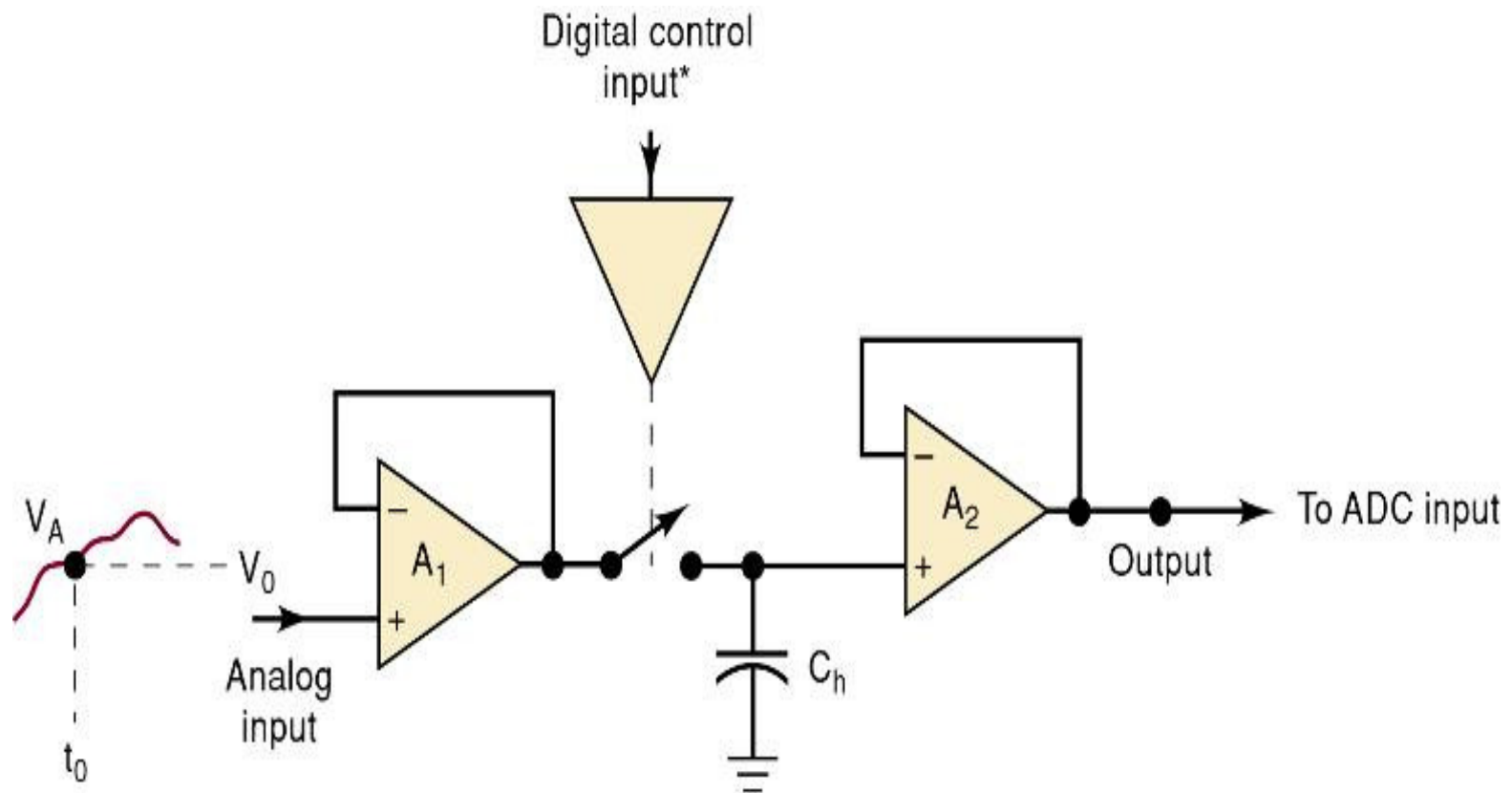
Simplified diagram of a sample-and-hold circuit.




*Control = 1 \rightarrow switch closed \rightarrow sample mode
Control = 0 \rightarrow switch open \rightarrow hold mode

Applications of Analog Interfacing

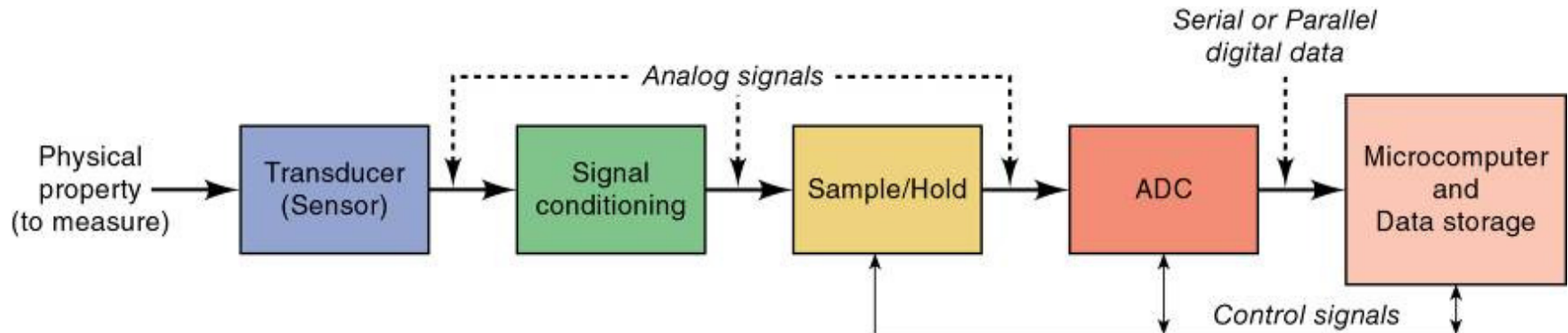Block diagram of a data acquisition system.



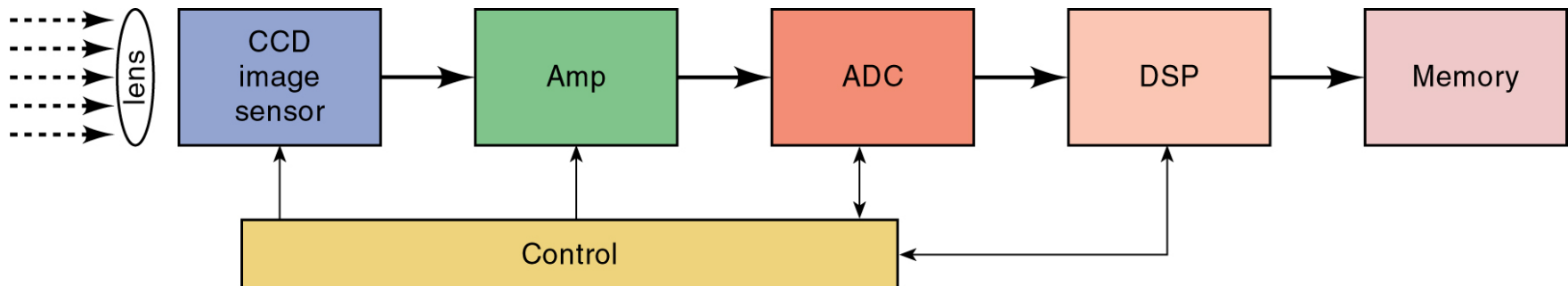- A familiar application that interfaces analog devices to a digital system is a digital camera.
 - Transducer typically a charge-coupled device (CCD).
- Analog signals are read out of the CCD by shifting the electric charges through successive capacitors under the control of drivers and timing circuits.
 - Amplified (signal conditioning) and then digitized by the ADC.



- The DSP block applies image signal-processing algorithms to the digital data before storing the information in a memory device.
 - Data are usually compressed.
- **Data compression** is the process of encoding information with fewer bits representing the data.
 - Only works when both the sender and receiver of the information understand the specific encoding scheme.

