

# *Operational Amplifiers (Op-Amp)*

## Background

- **Originally invented in early 1940s using vacuum tube technology**

Initial purpose was to execute math operations in analog electronic calculating machines

- **Shrunk in size with invention of transistor**

- **Most now made on integrated circuit (IC)**


Only most demanding applications use discrete components

- adding signals
- subtracting signals
- integrating signals

- **Huge variety of applications, low cost, and ease of mass production make them extremely popular**
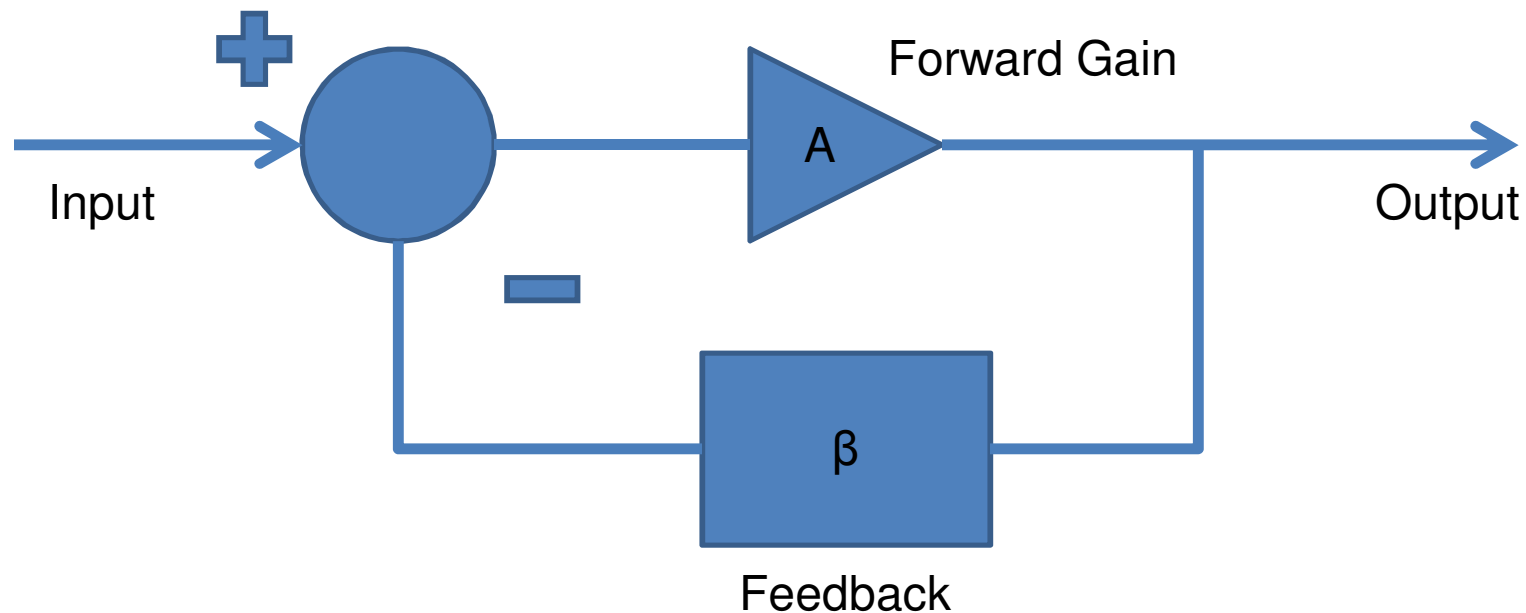
## History of the Op-Amp – The Dawn

- Before the Op-Amp: Harold S. Black develops the feedback amplifier for the Western Electric Company (1920-1930)




# Introduction

- An Operational Amplifier (Op-Amp) is an integrated circuit that uses external voltage to amplify the input through a very high gain.
  - We recognize an Op-Amp as a mass-produced component found in countless electronics.
- *Operational Amplifier (OPAMP) is a very high gain amplifier fabricated on Integrated Circuit (IC)*
  - Finds application in
    - Audio amplifier : Speakers and microphone circuits in cell phones, computers, mp3 players, boom boxes, etc.
    - Signal generator
    - Signal filters
    - Power amplifiers
    - Biomedical Instrumentation : Biomedical systems including heart monitors and oxygen sensors.
  - Analog computers
    - Combination of integrators, differentiators, summing amplifiers, and multipliers
      - And numerous other applications

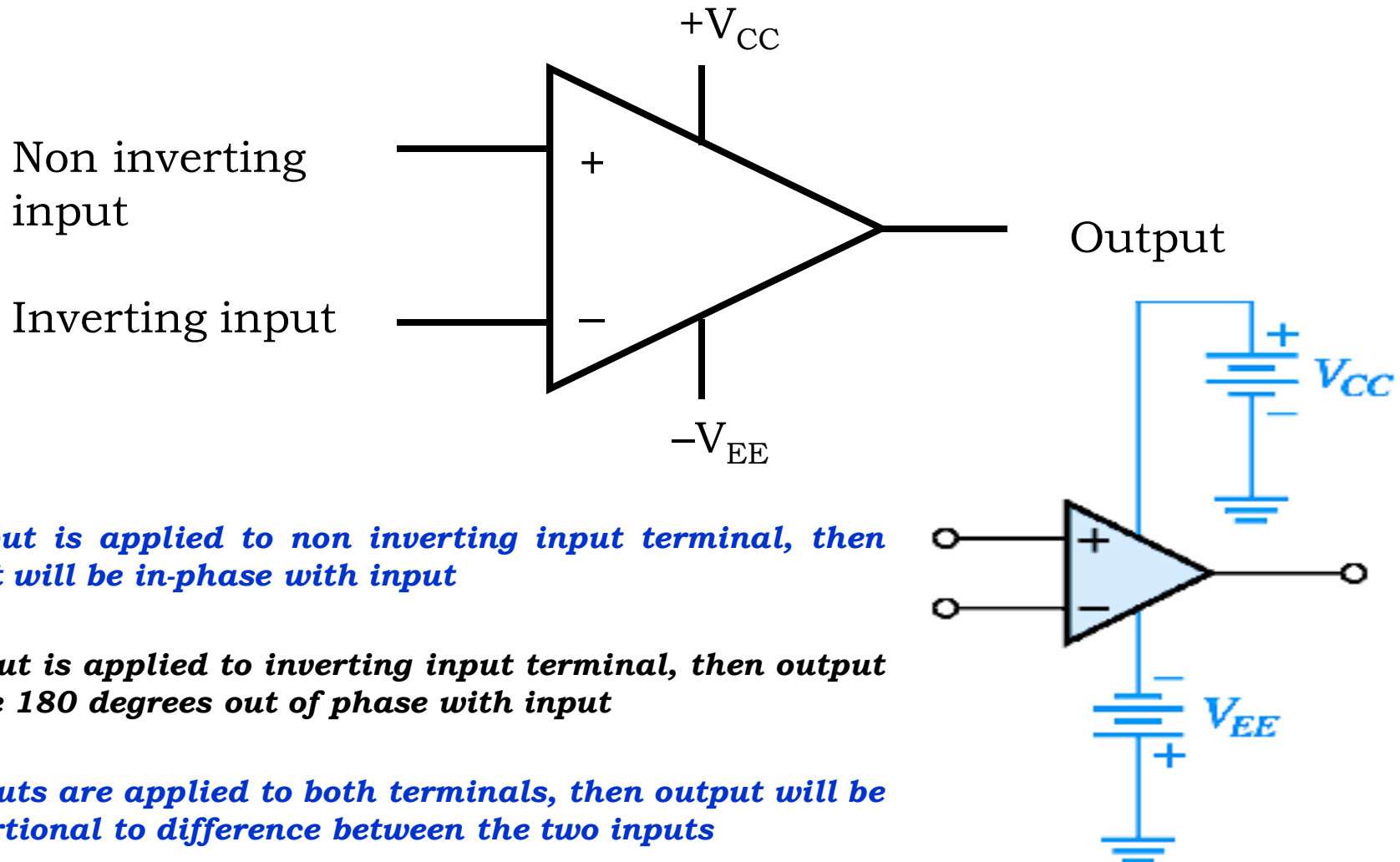
## What is an Op-Amp? – The Inside (OPAMP terminals)

*The actual count varies, but an Op-Amp contains several Transistors, Resistors, and a few Capacitors and Diodes.*

*For simplicity, an Op-Amp is often depicted as this:*




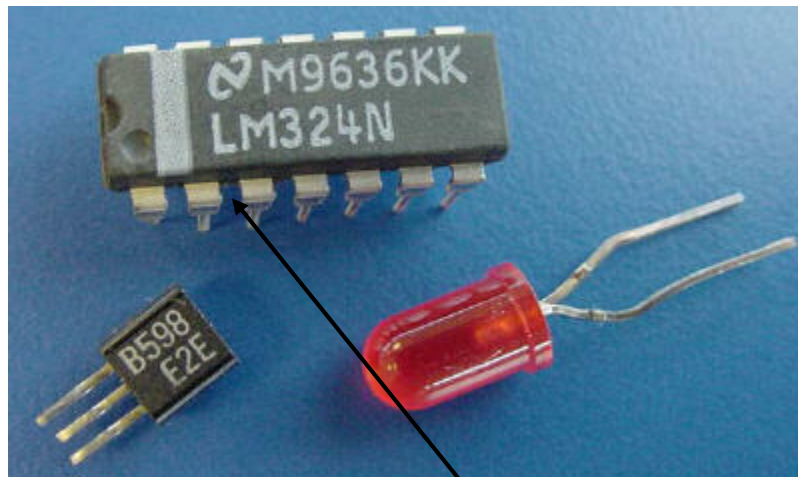- Two DC power supplies (dual) are required
- Magnitudes of both may be same
- The other terminal of both power supplies are connected to common ground
- All input and output voltages are measured with reference to the common ground



Integrated Circuit


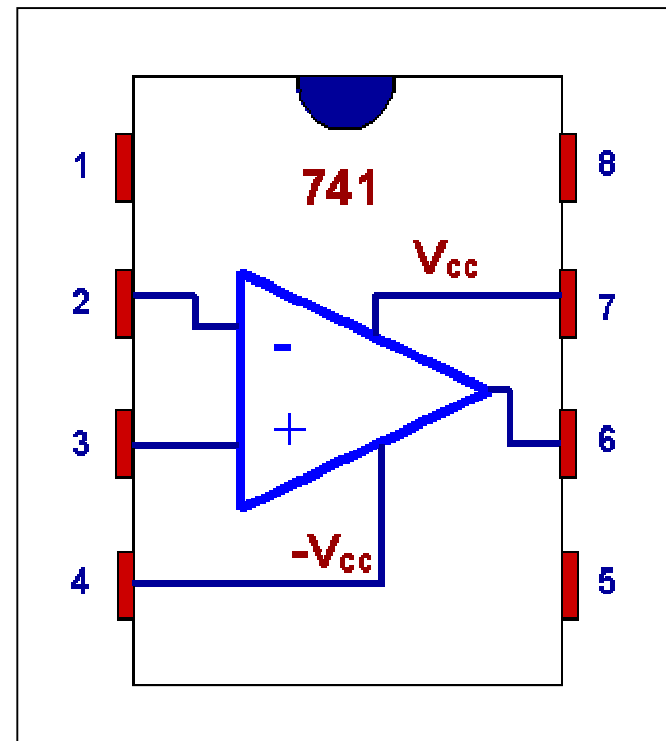
What an Op-Amp looks like to a lay-person




What an Op-Amp looks like to an engineer
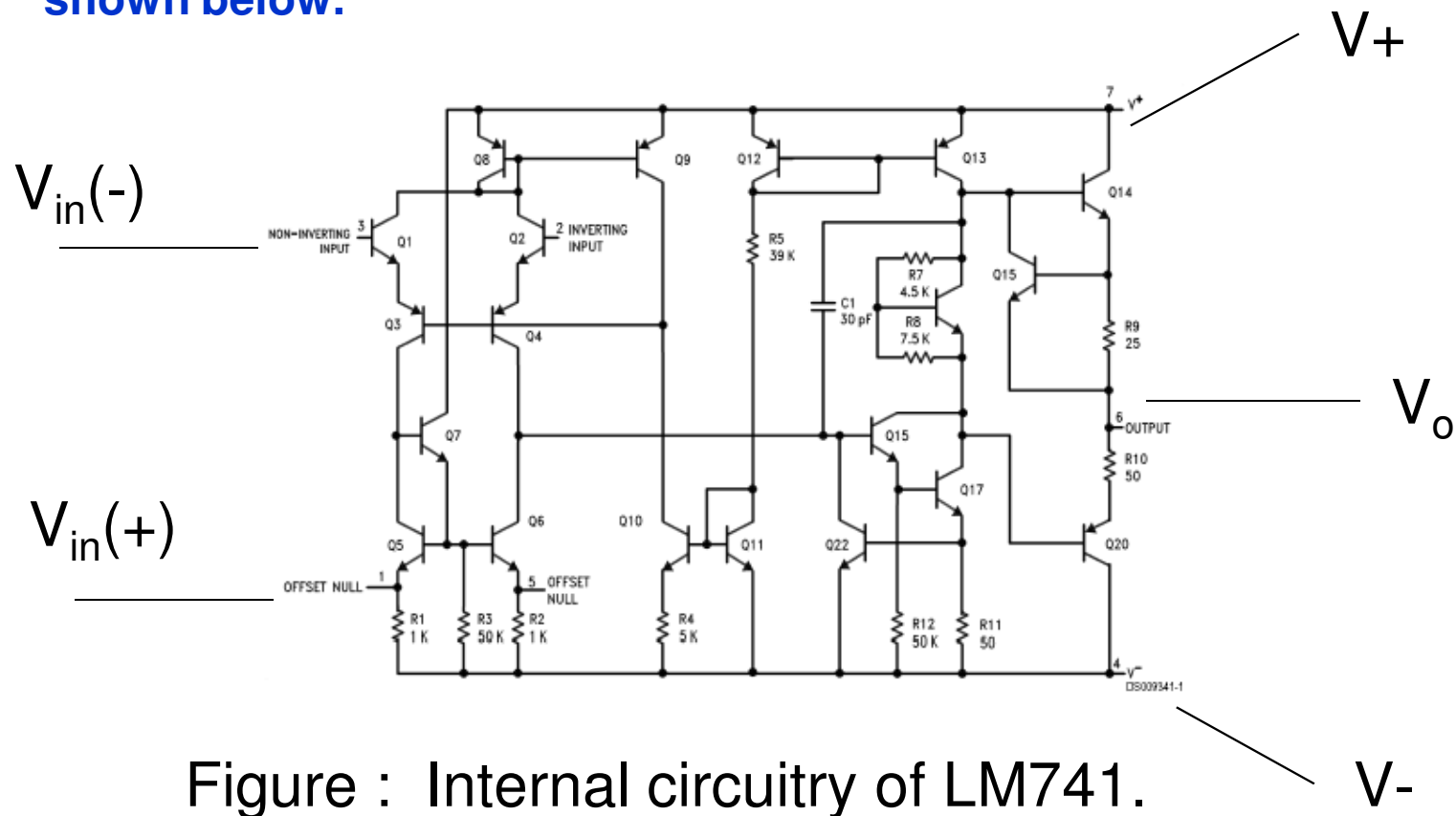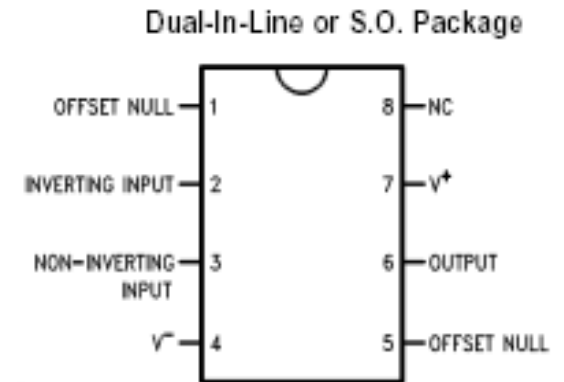
# Operational Amplifiers

The op amp is built using VLSI techniques. The circuit diagram of an LM 741 from National Semiconductor is shown below.



## Internal Block Diagram

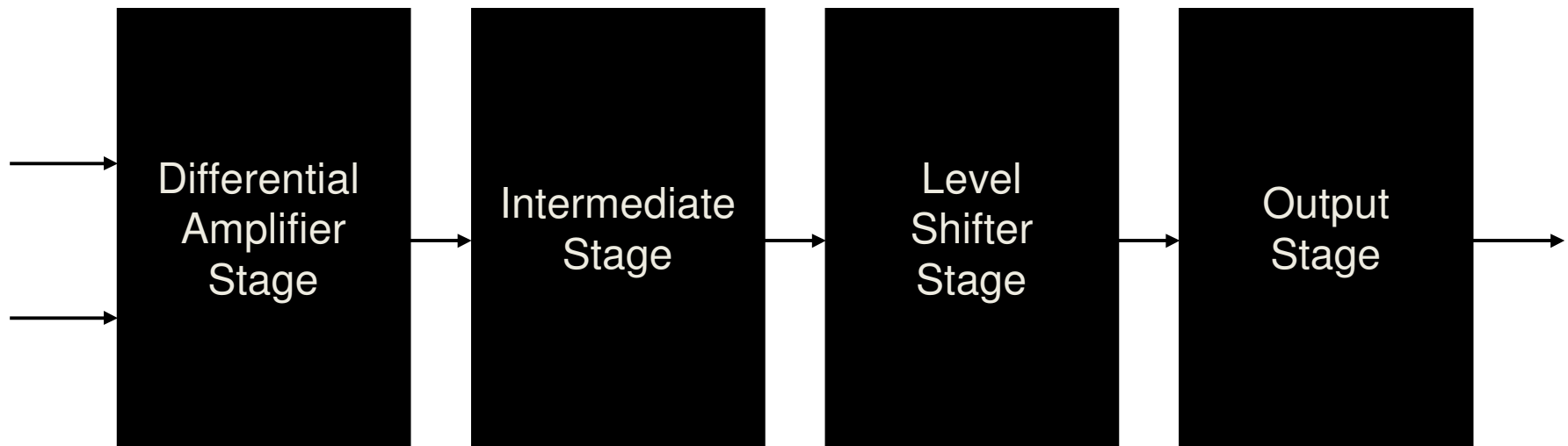

***Four stages can be identified –***

***Input stage or differential amplifier stage can amplify difference between two input signals; Input resistance is very high; Draws zero current from the input sources***




## *Cont...*

- **Intermediate stage (or stages) use direct coupling; provide very high gain**
- **Level shifter stage shifts the dc level of output voltage to zero (can be adjusted manually using two additional terminals)**
- **Output stage is a power amplifier stage; has very small output resistance; so output voltage is the same, no matter what is the value of load resistance connected to the output terminal**


## Ideal Operational Amplifier

- Ideal OPAMP
  - Infinite differential mode gain
  - Zero common mode gain
  - Infinite CMRR
  - Infinite input resistance
  - Zero output resistance
  - Infinite bandwidth
  - Infinite slew rate
  - Zero input offset voltage
  - Zero input offset current
  - Zero output offset voltage

# Ideal OPAMP Circuit

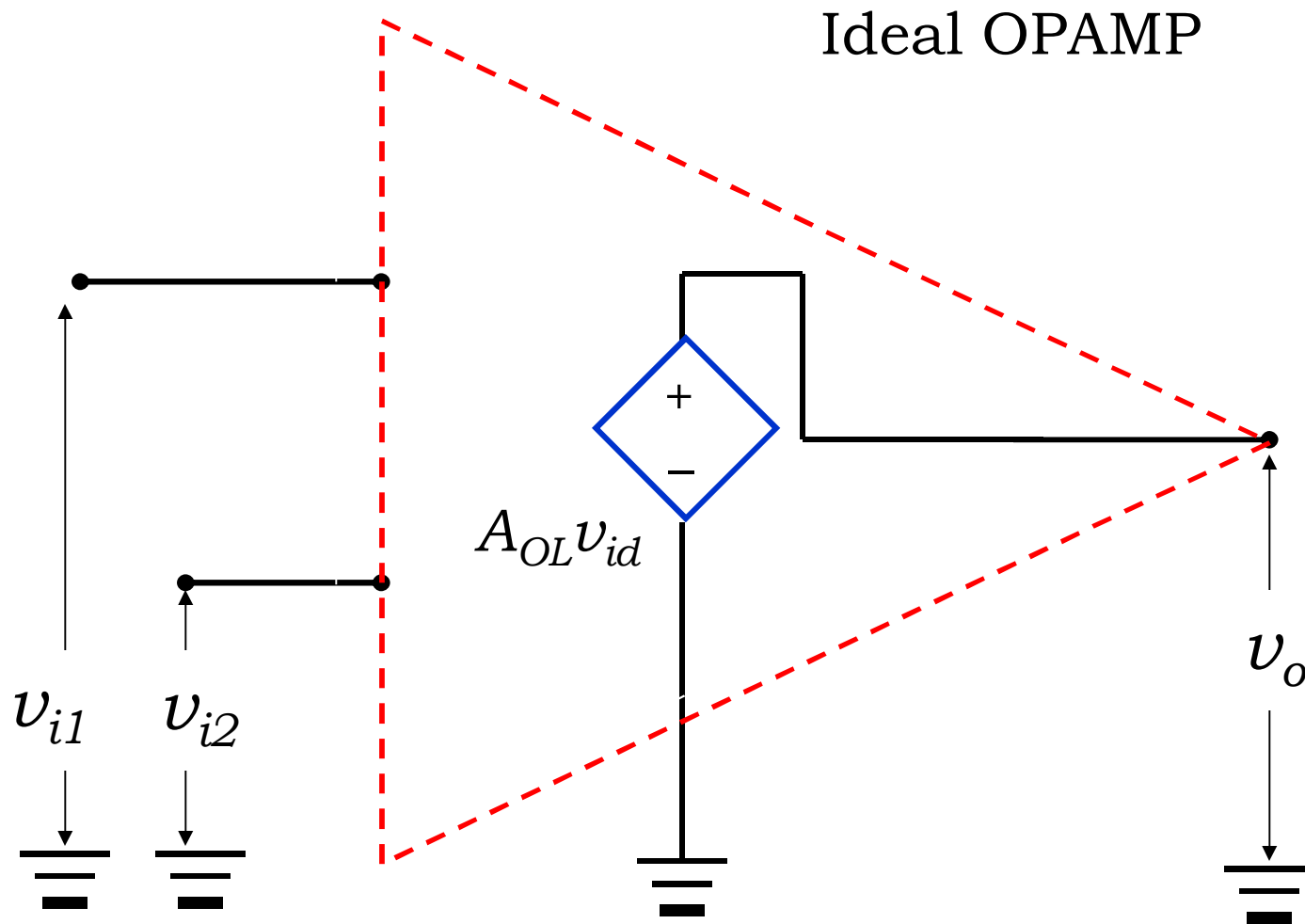


## Ideal Op Amp:

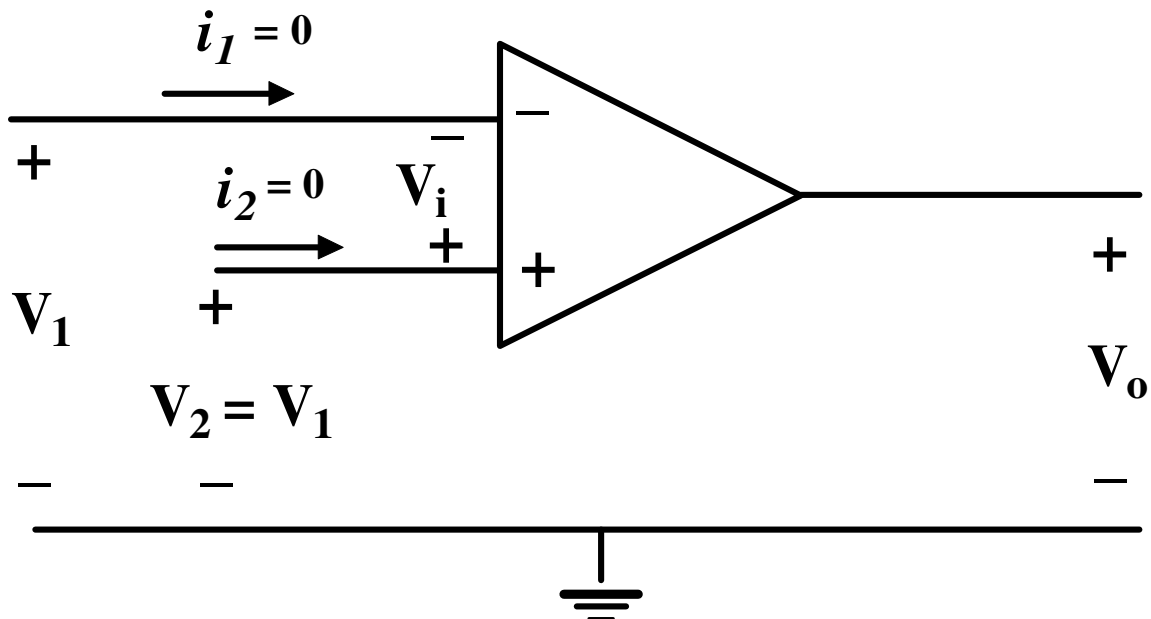

**Figure : Ideal op amp.**

- (a)  $i_1 = i_2 = 0$ : Due to infinite input resistance.
- (b)  $V_i$  is negligibly small;  $V_1 = V_2$ .

## Equivalent Circuit Of An Op Amp,

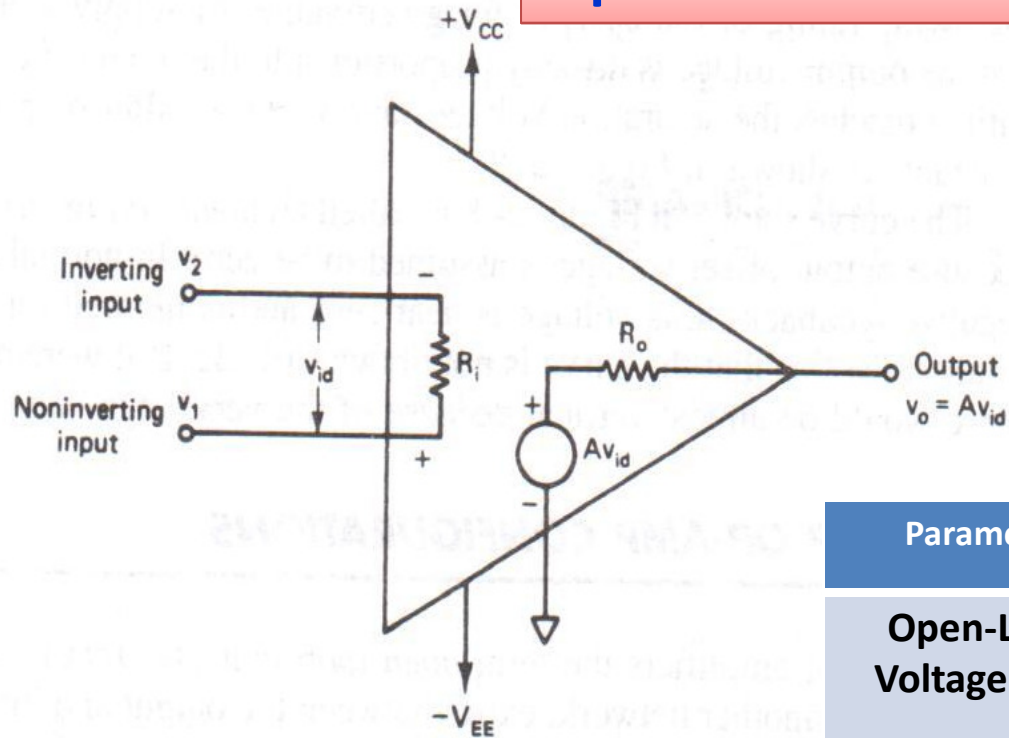


$$v_o = A v_{id} = A(v_1 - v_2)$$

where  $A$  = large-signal voltage gain

$v_{id}$  = difference input voltage

$v_1$  = voltage at the noninverting input terminal with respect to ground

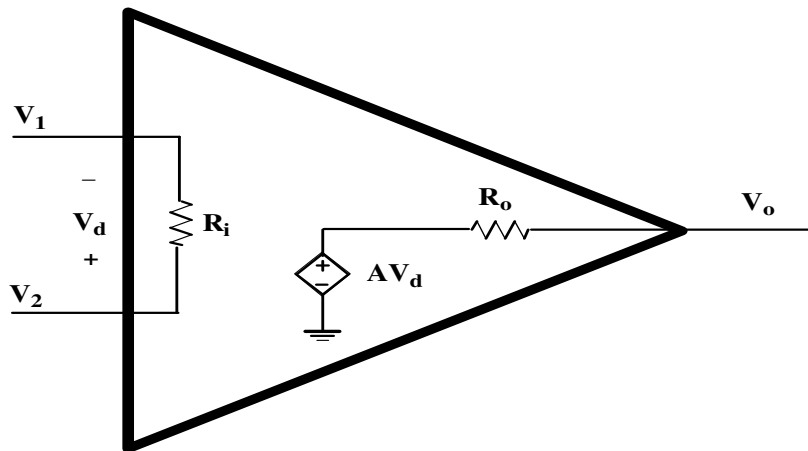$v_2$  = voltage at the inverting terminal with respect to ground



Parameter	Variable	Typical Ranges	Ideal Values
Open-Loop Voltage Gain	$A$	$10^5$ to $10^8$	$\infty$
Input Resistance	$R_i$	$10^5$ to $10^{13} \Omega$	$\infty \Omega$
Output Resistance	$R_o$	10 to $100 \Omega$	$0 \Omega$
Supply Voltage	$V_{CC}/V^+$ $-V_{CC}/V^-$	5 to 30 V -30V to 0V	N/A N/A

## OPAMP Characteristics

- **Differential mode gain  $A_d$** 
  - It is the factor by which the difference between the two input signals is amplified by the OPAMP
- **Common mode gain  $A_{cm}$** 
  - It is the factor by which the common mode input voltage is amplified by the OPAMP
- **Common mode rejection ratio  $CMRR$**   
Is the ratio of  $A_d$  to  $A_{cm}$  expressed in decibels
- **Input resistance  $R_i$**   
It is the equivalent resistance measured between the two input terminals of OPAMP
- **Output resistance  $R_o$**   
It is equivalent resistance measured between output terminal and ground
- **Bandwidth**  
It is the range of frequency over which the gain of OPAMP is almost constant
- **Output offset voltage  $V_{oo}$** 
  - It is the output voltage when both input voltages are zero
  - Denoted as  $V_{oo}$

## Cont...

- **Input offset voltage  $V_{io}$**

- It is the differential input voltage that must be applied at the input terminals in order to make output voltage equal to zero
- $V_{io} = |v_1 - v_2|$  for  $v_o = 0$

- **Input offset current  $I_{io}$**

It is the difference between the currents in the input terminals when both input voltages are zero

$$I_{io} = |I_1 - I_2| \quad \text{when } v_1 = v_2 = 0$$

- **Input bias current  $I_{ib}$**

It is the average of the currents in the input terminals when both input voltages are zero

$$I_{ib} = (I_1 + I_2) / 2 \quad \text{when } v_1 = v_2 = 0$$

- **Slew rate  $SR$**

It is the maximum rate of change of output voltage with respect to time

Slew rate has to be very high if OPAMP has to operate efficiently at high frequencies

- **Supply voltage rejection ratio  $SVRR$**

It is the maximum rate at which input offset voltage of OPAMP changes with change in supply voltage