

# **Assignment for Applied Electronics**

(Due Date 30/5/2014 at 5 P.M)


## ***(Part A- Digital Electronics)***

- 1) Note difference between CPLD and FPGA.
- 2) Convert
  - a) Decimal to Binary- 77, 96, 0.63
  - b) Binary to Decimal – 1010, 001000010
  - c) Hex to Binary- 9124,F44H
  - d) Decimal to Hex- 99,1100,123
- 3) Find 2's Complement
  - a) 1001010
  - b) 111001
- 4) Perform –
  - a) 23D9 + 94BE
  - b) 59F - 2B8
  - c) 11010011 + 01101111
- 5) Explain and write down Purpose of Using Gray Code, Excess3 Code, ASCII Code.
6. Convert the decimal number 345 to binary in two ways: (a) convert directly to binary; (b) convert first to hexadecimal, then from hexadecimal to binary, Which method is faster?
- 7) Suppose 8 bit word in memory is 11000010. Using hamming algorithm what check bits would be stored in memory.
- 8) Implement  $x'y'z + x'yz + xy'$  using OR, AND & NOT Gate.
- 9) Make AND & OR Gates using Diodes.
- 10) What are essential and non essential prime implicant in k map. Explain with examples
- 11) Simplify using k map
$$F = x'y'z + xy'z + xyz' + xyz$$
- 12) Implement using 8:1 MUX and 4:1 MUX
$$F = x'y'z + xy'z + xyz' + xyz$$
- 13) What is racing in sequential circuits and how it can be avoided.
- 14) Convert JK Flip Flop into D and T Flip flop.


## (Part B- Analog Electronics)

- 1) Explain in detail the working of full wave rectifier and derive the expression for maximum rectifying efficiency.

 - 2) Determine  $V_o$  for each network of as given below with the input shown




 - 3) Determine  $V_o$  for each network of as given below with the input shown



- 4) Explain in detail (with circuit diagram) BJT circuit configurations and compare them.

 - 5) In the circuit shown below in Fig.,  $R_1=12\text{ k}\Omega$ ,  $R_2 = 5\text{ k}\Omega$ ,  $R_3 = 8\text{ k}\Omega$ ,  $R_F = 12\text{ k}\Omega$ . The inputs are:  $V_1 = 9\text{ V}$ ,  $V_2 = -3\text{ V}$  and  $V_3 = -1\text{ V}$ . Compute the output voltage



- 6) What is a load line and how is it used in the calculation of current and voltage gains for a single stage amplifier?

- 7) Explain how an opamp can be used as

a) Integrator

b) Differentiator

- 8) Calculate the dc bias, voltage gain, input impedance, output impedance and resulting output voltage for the cascade amplifier shown in Fig. Calculate the load voltage if a  $10\text{ k}\Omega$  load is connected across the output. Given  $V_{GSQ} = -1.9\text{V}$ ,  $I_{DQ} = 2.8\text{mA}$ .


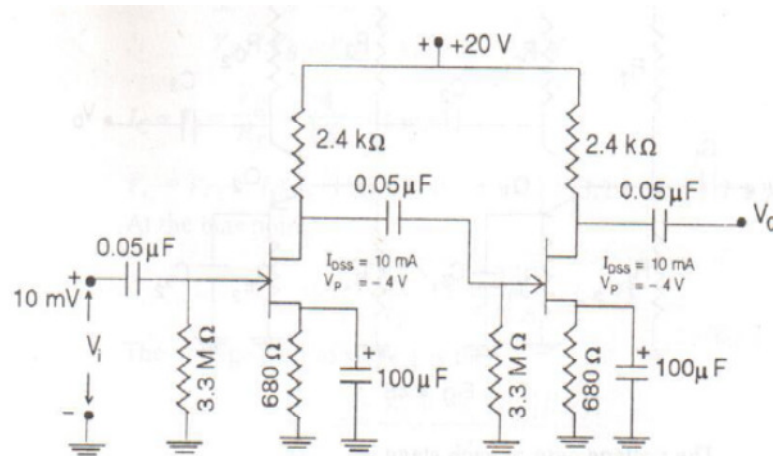


Fig.

 - 9) Determine the suitable resistor values for the differential amplifier circuit in Fig.. The transistor parameters are  $h_{fe} = 60$  and  $h_{ie} = 1.4\text{ k}\Omega$ .



- 10.) Calculate the closed-loop gain for the negative feedback amplifier shown in Fig. Also calculate the closed loop gain when the open loop gain is changed by  $\pm 50\%$ . Note that  $A_v = 100\,000$  and  $B = 1/100$ .

