


# **Sequential Circuits (Circuits as Memory )**

## Sequential Circuits

- Most digital systems like digital watches, digital phones, digital computers, digital traffic light controllers and so on require memory elements
- Memory elements are digital circuits that can store and retrieve data in the form of 1's and 0's.
- The output of the systems with memory depends not only on present inputs but also on what has happened in the past.
- SR latch is an example of memory circuits that can store one bit of information

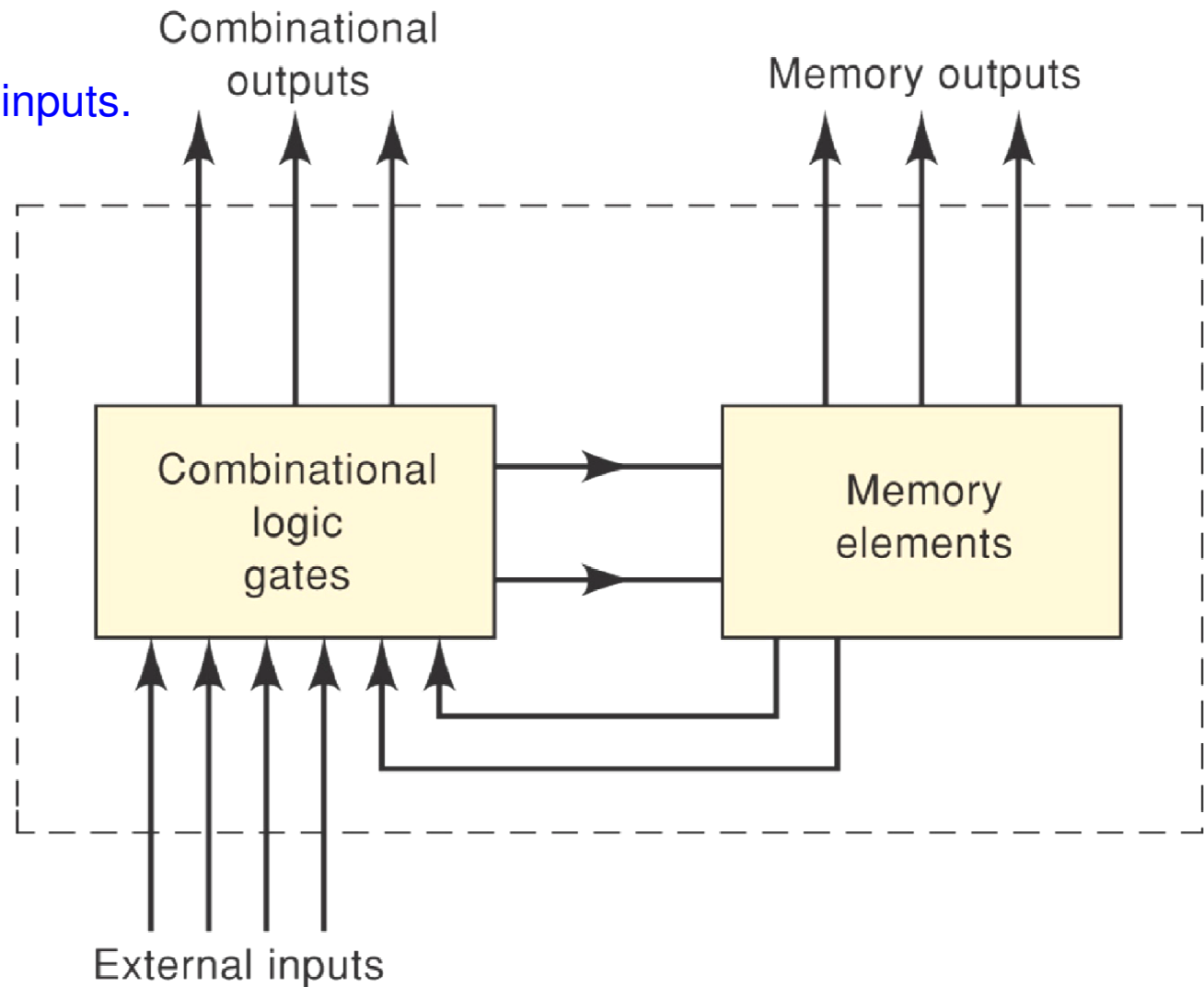
# General Digital System

Outputs depend on:  
current inputs, previous inputs.


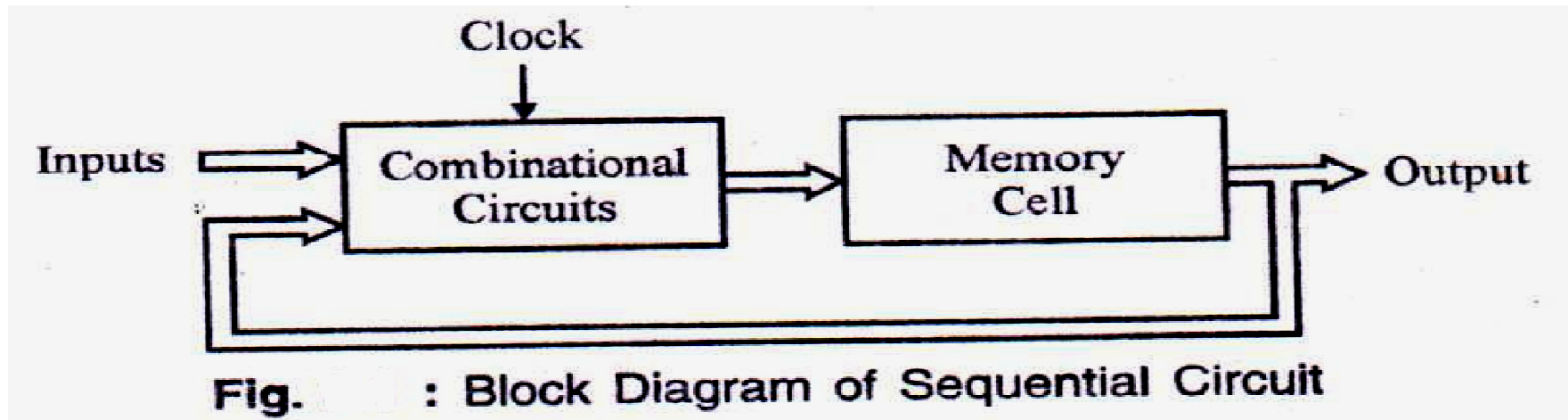
## Cont.....Sequential circuit

•These circuits form a **sequential circuit**, because the output of the circuit is also used as input to the circuit.




## Sequential circuit

The output is a function of the input values and the existing state of the circuit.

**We describe the circuit operations using**


- Boolean expressions
- Logic diagrams
- Truth tables

# Sequential Circuits

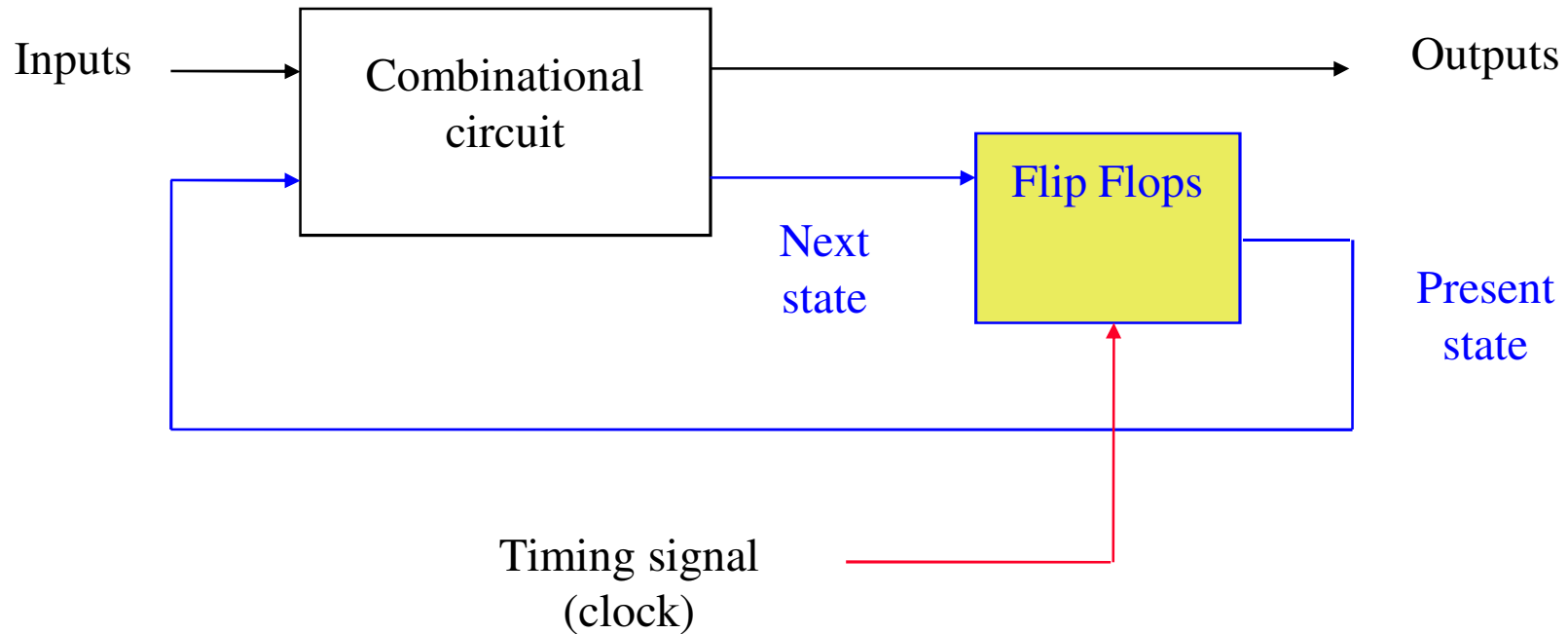


## **Clock**

a periodic external event (input)

 

synchronizes when current state changes happen  
keeps system well-behaved  
makes it easier to design and build large systems
 
## General flip-flop symbol and definition of its two possible output states



### Output states

$Q = 1, \bar{Q} = 0$ : called HIGH or 1 state; also called SET state

$Q = 0, \bar{Q} = 1$ : called LOW or 0 state; also called CLEAR or RESET state

(b)

## NAND Gate Latch



- The NAND gate latch or simply latch is a basic FF.
- The inputs are set and clear (reset)
- The inputs are active low, that is, the output will change when the input is pulsed low.
- When the latch is set

$$Q = 1 \text{ and } \bar{Q} = 0$$

- When the latch is clear or reset

$$Q = 0 \text{ and } \bar{Q} = 1$$

  A NAND latch is an example of a bistable device

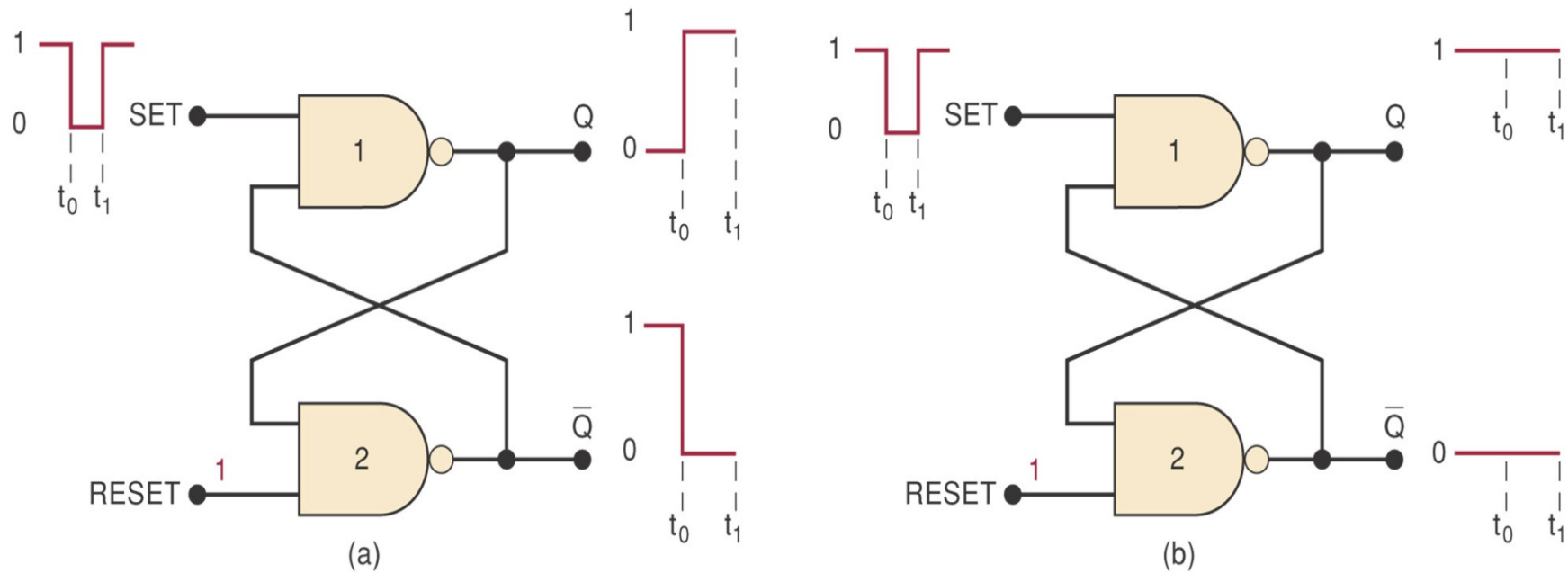


**Figure** A NAND latch has two possible resting states when SET = RESET = 1.

NAND		
0	0	1
0	1	1
1	0	1
1	1	0



## Setting the NAND Flip-Flop

 


**Figure** Pulsing the SET input to the 0 state when (a)  $Q = 0$  prior to SET pulse; (b)  $Q = 1$  prior to SET pulse. Note that, in both cases,  $Q$  ends up HIGH.

NAND


0	0	1
0	1	1
1	0	1
1	1	0

## Resetting the NAND Flip-Flop



**Figure** Pulsing the RESET input to the LOW state when (a)  $Q = 0$  prior to RESET pulse; (b)  $Q = 1$  prior to RESET pulse. In each case,  $Q$  ends up LOW.

# Function table of a NAND latch

 


(a)

Set	Reset	Output
1	1	No change
0	1	Q = 1
1	0	Q = 0
0	0	Invalid*

\*Produces  $Q = \overline{Q} = 1$ .


(b)

 


## NAND Gate Latch Summary

- **Summary of the NAND latch:**
- **SET = RESET = 1.** Normal resting state, outputs remain in state prior to input.
- **SET = 0, RESET = 1.** Q will go high and remain high even if the SET input goes high.
- **SET = 1, RESET = 0.** Q will go low and remain low even if the RESET input goes high.
- **SET = RESET = 0.** Output is unpredictable because the latch is being set and reset at the same time.
 
### Other Representations of a NAND latch




(a)

 

(b)


## NOR Gate Latch

- The NOR latch is similar to the NAND latch except that the outputs are reversed.
- The SET and RESET inputs are active high, that is, the output will change when the input is pulsed high.
- In order to ensure that a FF begins operation at a known level, a pulse may be applied to the SET or RESET inputs when a device is powered up.

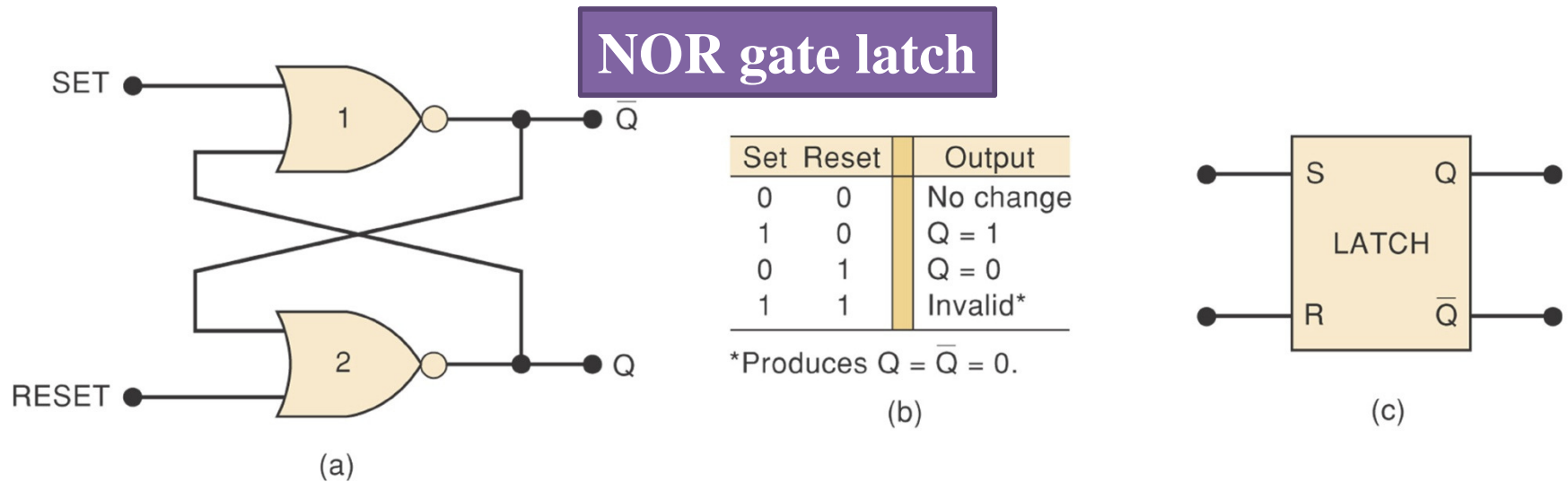

**Figure** (a) NOR gate latch; (b) function table; (c) simplified block symbol.


 
**Determine Q for a NOR latch given the inputs below**



# Digital Pulses


- The transition from low to high on a positive pulse is called rise time ( $t_r$ ).
  - Rise time is measured between the 10% and 90% points on the leading edge of the voltage waveform.
- The transition from high to low on a positive pulse is called fall time ( $t_f$ ).
  - Fall time is measured between the 90% and 10% points on the trailing edge of the voltage waveform.

## Rise and Fall times

  
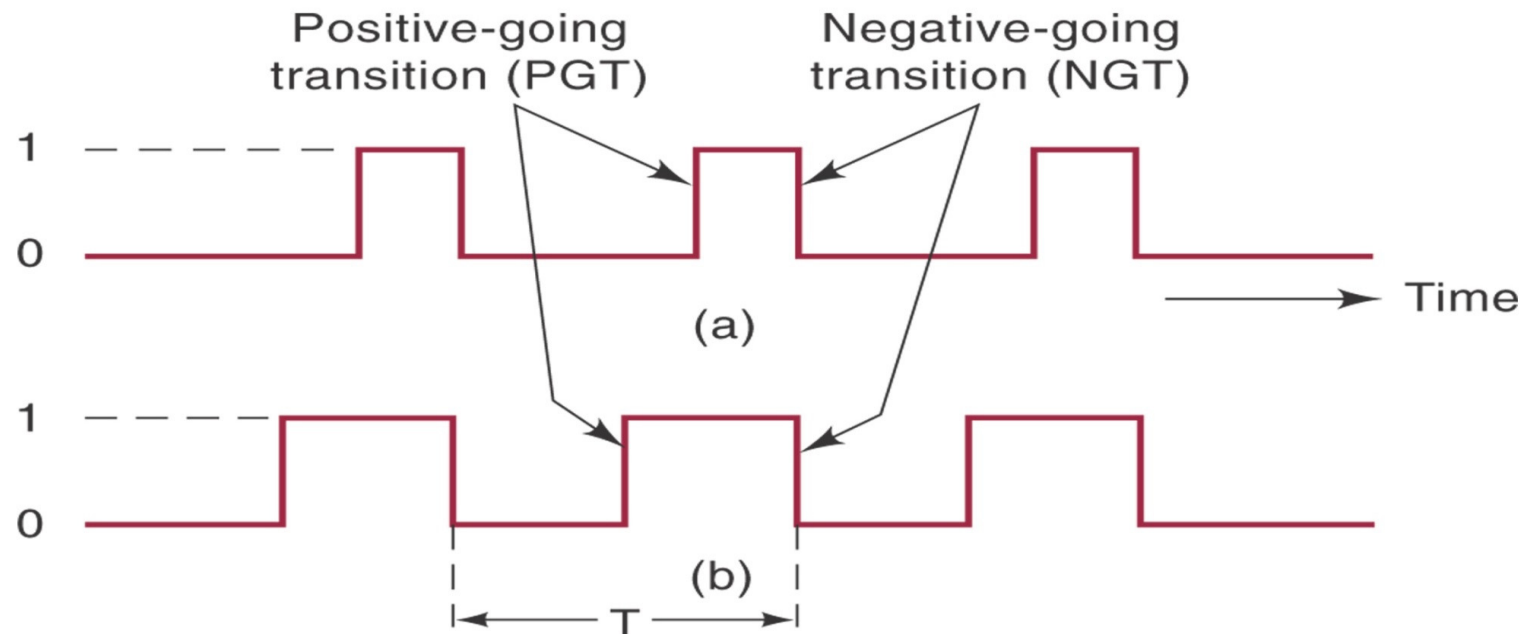
## Clock Signals and Clocked Flip-Flops

- **Asynchronous** system – outputs can change state at any time the input(s) change.
- **Synchronous** system – output can change state only at a specific time in the clock cycle.
  - The clock signal is a rectangular pulse train or square wave.
  - Positive going transition (PGT) – when clock pulse goes from 0 to 1.
  - Negative going transition (NGT) – when clock pulse goes from 1 to 0.
  - Transitions are also called edges.






## Clock Signals and Clocked Flip-Flops

- **Clocked FFs change state on one or the other clock transitions.**
- **Some common characteristics:**
  - Clock inputs are labeled CLK, CK, or CP.
  - A **small triangle** at the CLK input indicates that the input is activated with a **PGT**.
  - A **bubble and a triangle** indicates that the CLK input is activated with a **NGT**.
  - Control inputs have an effect on the output only at the active clock transition (NGT or PGT). These are also called synchronous control inputs.
  - The control inputs get the FF outputs ready to change, but the change is not triggered until the CLK edge.

 
## Clocked S-R Flip-Flop

- The SET-RESET (or SET-CLEAR) FF will change states at the positive going or negative going clock edge.



Inputs			Output
S	C	CLK	Q
0	0	↑	$Q_0$ (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	Ambiguous

 $Q_0$  is output level prior to ↑ of CLK.  
↓ of CLK produces no change in Q.



(a) Logic diagram

C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$ ; Reset state
1	1	0	$Q = 1$ ; set state
1	1	1	Indeterminate


(b) Function table

- Occasionally, desirable to avoid latch changes
- C = 0** disables all latch state changes
- Control signal **enables** data change when **C = 1**
- Right side of circuit same as ordinary S-R latch.

Fig. SR Latch with Control Input

## Clocked SR Flip-Flop


**Figure (a)** Clocked S-R flip-flop that responds only to the positive-going edge of a clock pulse; (b) function table; (c) typical waveforms.

 


Inputs			Output
S	R	CLK	Q
0	0	↑	$Q_0$ (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	Ambiguous

$Q_0$  is output level prior to ↑ of CLK.  
↓ of CLK produces no change in Q.

(b)

 

Inputs			Output
S	R	CLK	Q
0	0	↓	$Q_0$ (no change)
1	0	↓	1
0	1	↓	0
1	1	↓	Ambiguous

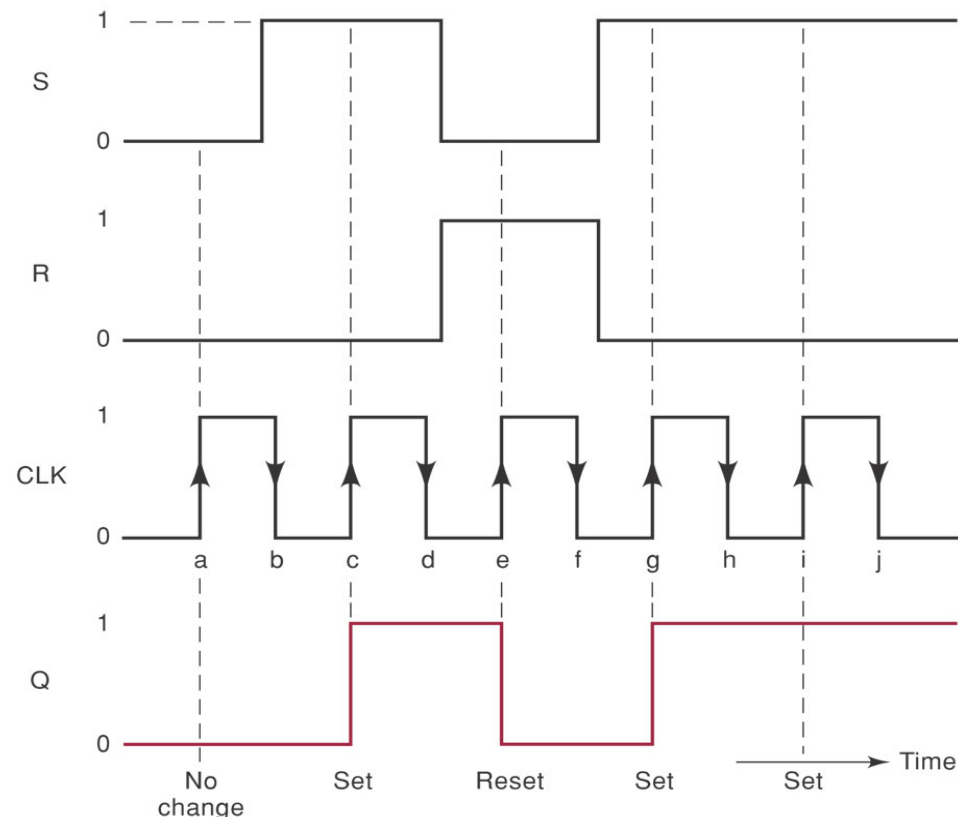


**Figure** Clocked S-R flip-flop that triggers only on negative-going transitions.
 
## Clocked J-K Flip-Flop

- Operates like the S-R FF. J is set, K is clear.
- When J and K are both high the output is toggled from whatever state it is in to the opposite state.
- May be positive going or negative going clock trigger.
- Has the ability to do everything the S-R FF does, plus operate in toggle mode.


## Clocked JK Flip-Flop



J	K	CLK	Q
0	0	↑	$Q_0$ (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	$\overline{Q_0}$ (toggles)

(a)

**Figure** (a) Clocked J-K flip-flop that responds only to the positive edge of the clock; (b) waveforms.

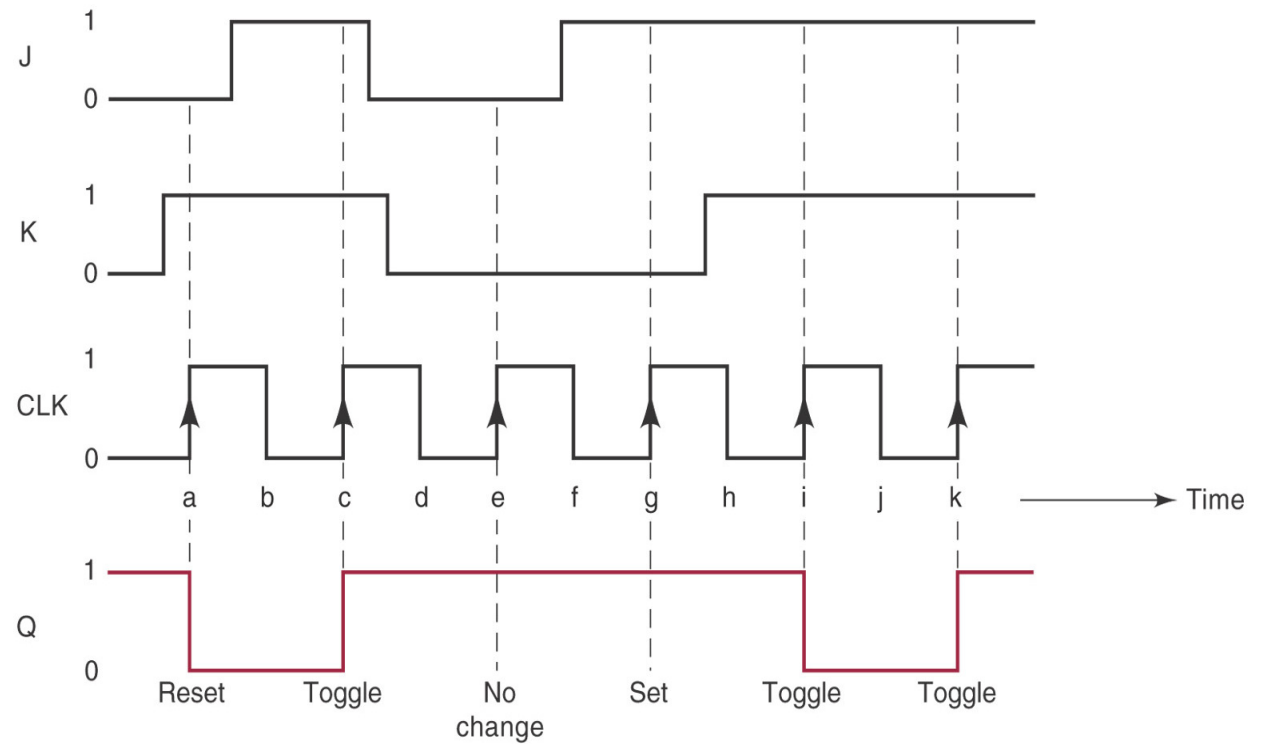


(b)

# J-K Flip-flop

The 4 modes of operation are:  
hold, set, reset, toggle



J	K	Q	Q'	Mode
0	0	Q	Q'	Hold
1	0	1	0	Sets
0	1	0	1	Resets
1	1	Q'	Q	Toggle

 

JK contains an internal  
**Active Low SR latch.**

## Mode of Operation: Hold



**Hold:** no change in Q.

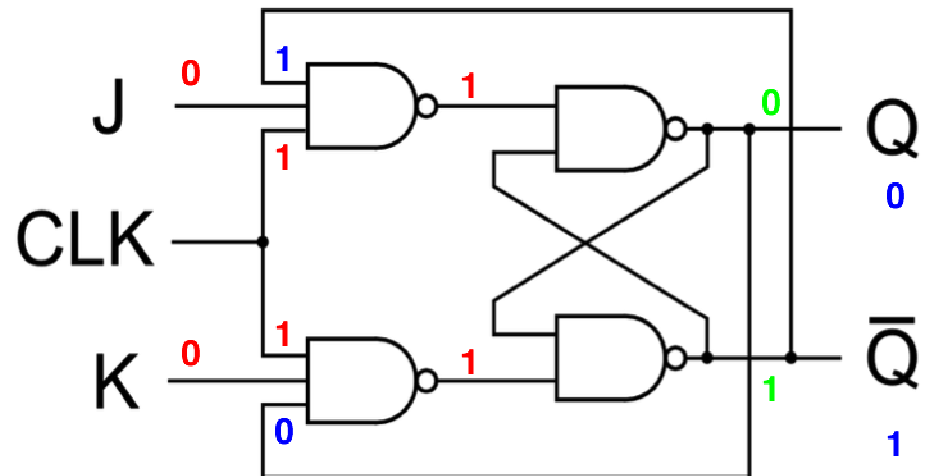 

J	K	Q	Q'	Orig. Q	Orig. Q'
0	0	0	1	0	1

## Mode of Operation: Set

**Set:**  $Q = 1$ .

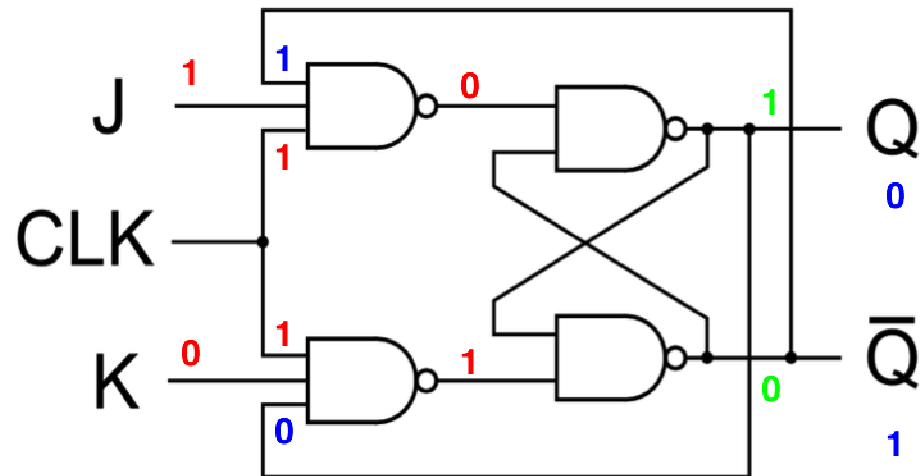
 


J	K	Q	Q'	Orig. Q	Orig. Q'
1	0	1	0	0	1



## Mode of Operation: Reset



**Reset:**  $Q = 0$ .

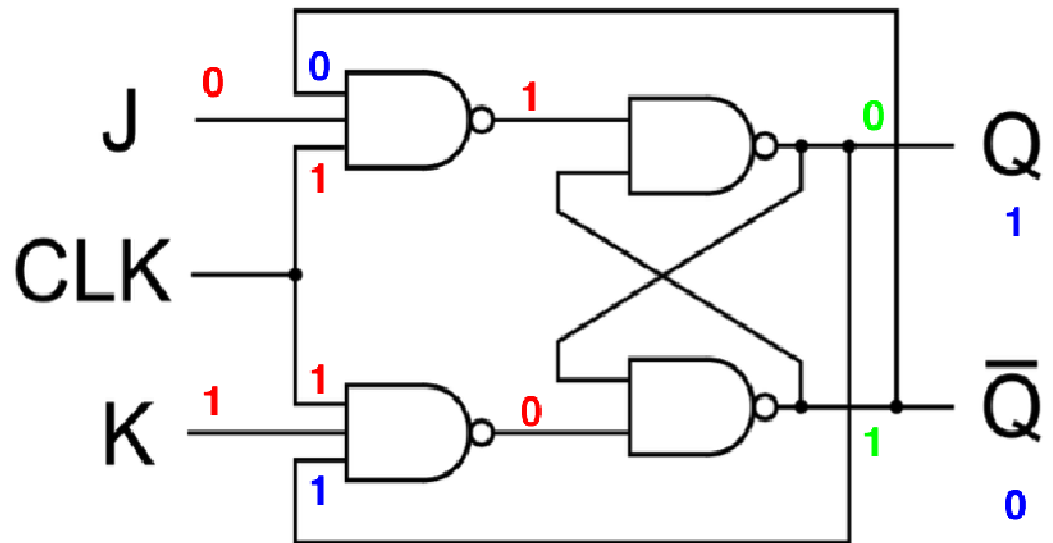 

J	K	Q	Q'	Orig. Q	Orig. Q'
0	1	0	1	1	0

## Mode of Operation: Toggle



**Toggle:**  $Q = Q'$ .

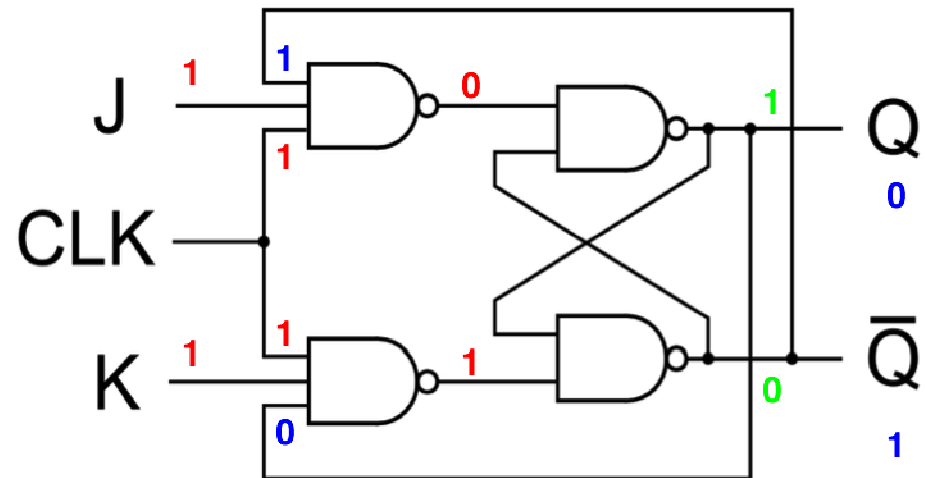 

J	K	Q	Q'	Orig. Q	Orig. Q'
1	1	1	0	0	1

## Mode of Operation: Toggle again


**Toggle:**  $Q = Q'$ .

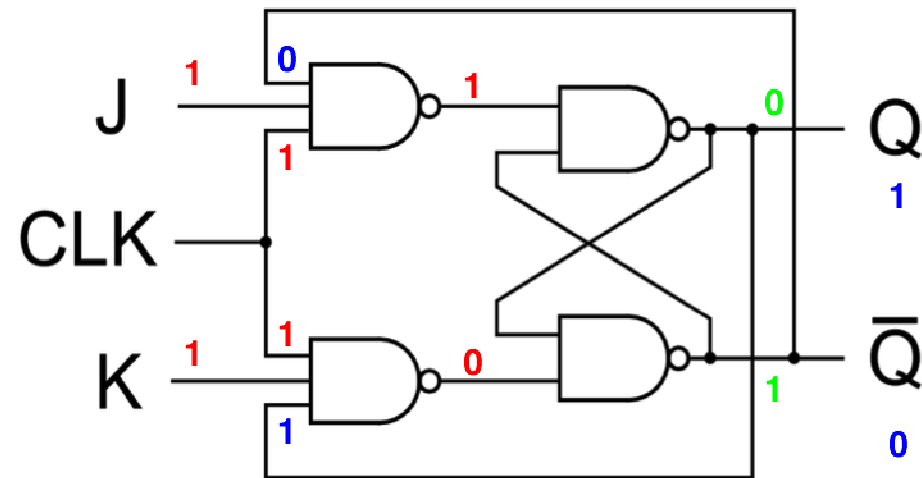 

J	K	Q	Q'	Orig. Q	Orig. Q'
1	1	0	1	1	0

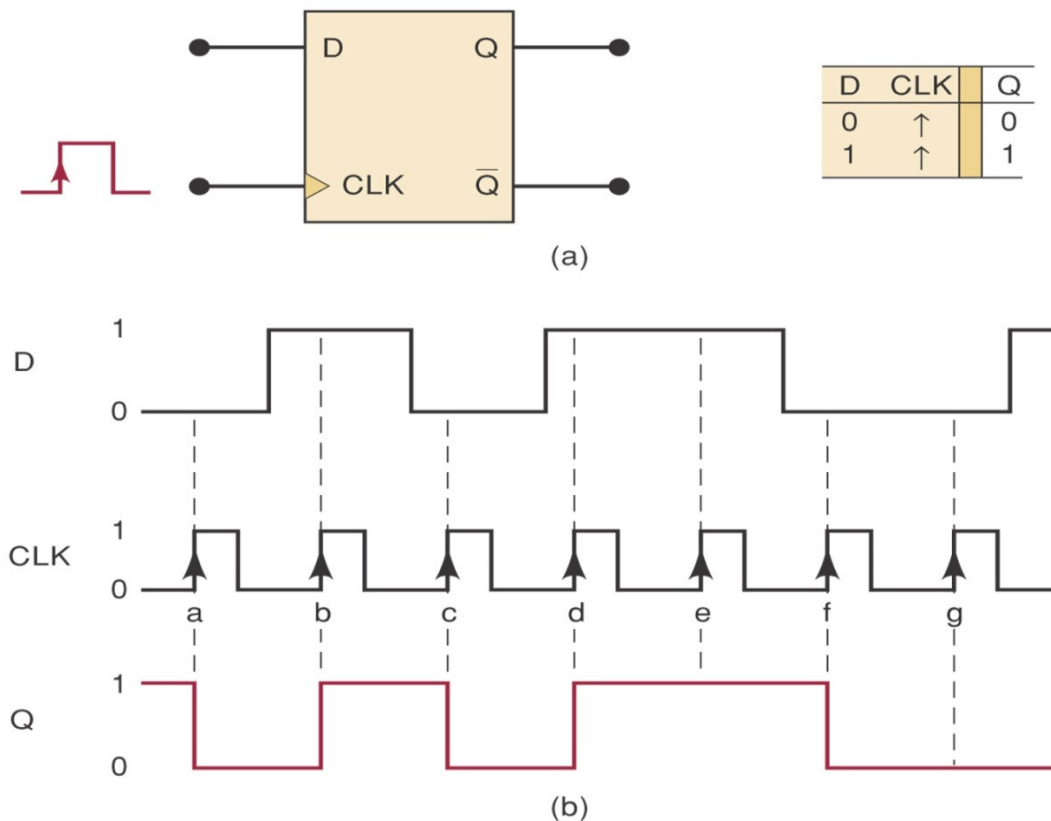
## Clocked D Flip-Flop

- One data input.
- The output changes to the value of the input at either the positive going or negative going clock trigger.
- May be implemented with a J-K FF by tying the J input to the K input through an inverter.
- Useful for parallel data transfer.



Edge-triggered D flip-flop

## D (Delay) Flip Flop

 

D	C	Q	Q'
0	1	0	1
1	1	1	0
X	0	Q <sub>0</sub>	Q <sub>0</sub> '


S	R	C	Q	Q'	
0	0	1	Q <sub>0</sub>	Q <sub>0</sub> '	Store
0	1	1	0	1	Reset
1	0	1	1	0	Set
1	1	1	1	1	Disallowed
X	X	0	Q <sub>0</sub>	Q <sub>0</sub> '	Store

When C is high, D passes from input to output (Q)

## Asynchronous Inputs

- Inputs that depend on the clock are synchronous.
- Most clocked FFs have asynchronous inputs that do not depend on the clock.
- The labels PRE and CLR are used for asynchronous inputs.
- Active low asynchronous inputs will have a bar over the labels and inversion bubbles.
- If the asynchronous inputs are not used they will be tied to their inactive state.
 
## Clocked J-K flip-flop with asynchronous inputs





J	K	Clk	$\overline{\text{PRE}}$	$\overline{\text{CLR}}$	Q
0	0	↓	1	1	Q (no change)
0	1	↓	1	1	0 (Synch reset)
1	0	↓	1	1	1 (Synch set)
1	1	↓	1	1	$\bar{Q}$ (Synch toggle)
x	x	x	1	1	Q (no change)
x	x	x	1	0	0 (asynch clear)
x	x	x	0	1	1 (asynch preset)
x	x	x	0	0	(Invalid)
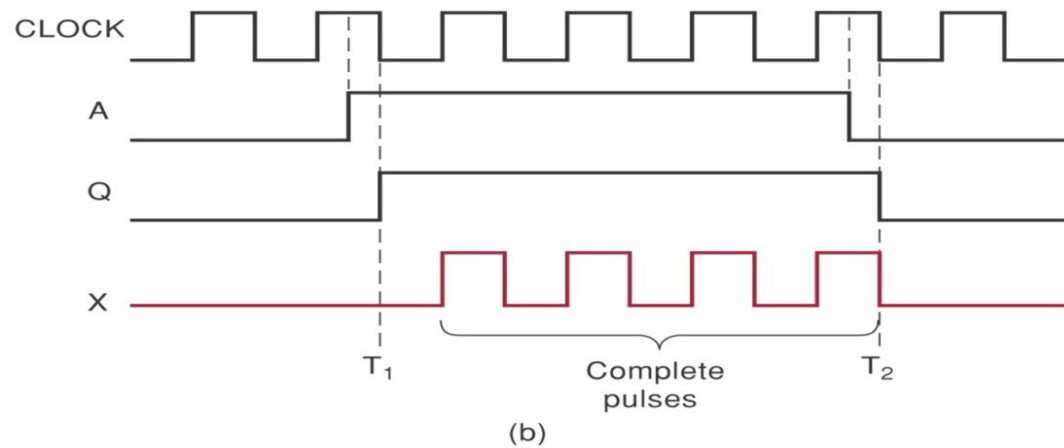 
## Flip-Flop Synchronization

- Most systems are primarily synchronous in operation, in that changes depend on the clock.
- Asynchronous and synchronous operations are often combined.
- The random nature of asynchronous inputs can result in unpredictable results.

The signal *A* has no effect until negative edge of clock.



**Edge-triggered flip-flop can Synchronize Circuit**

## Master-Slave D Flip Flop

- Consider two latches combined together
- Only one  $C$  value active at a time
- Output changes on **falling** edge of the clock


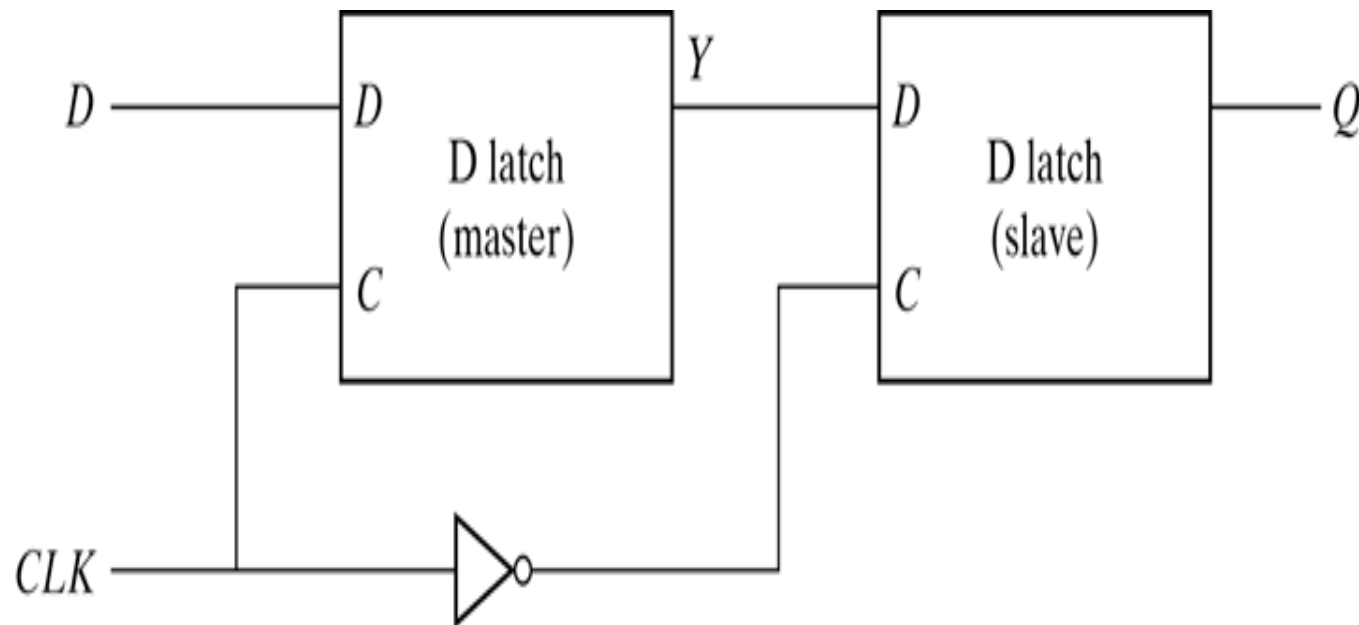


Fig. Master-Slave  $D$  Flip-Flop

- Stores a value on the positive edge of  $C$
- Input changes at other times have no effect on output

Positive edge triggered

 

D	C	Q	Q'
0	↑	0	1
1	↑	1	0
X	0	$Q_0$	$Q_0'$

D gets latched to Q on the rising edge of the clock.