

# INDUCTANCE AND CAPACITANCE




# Introduction




- Energy storage elements
- Passive
- Capacitance
  - ▣ Energy in electric fields
- Inductance
  - ▣ Energy in magnetic fields


# Parallel Plate Capacitor Construction

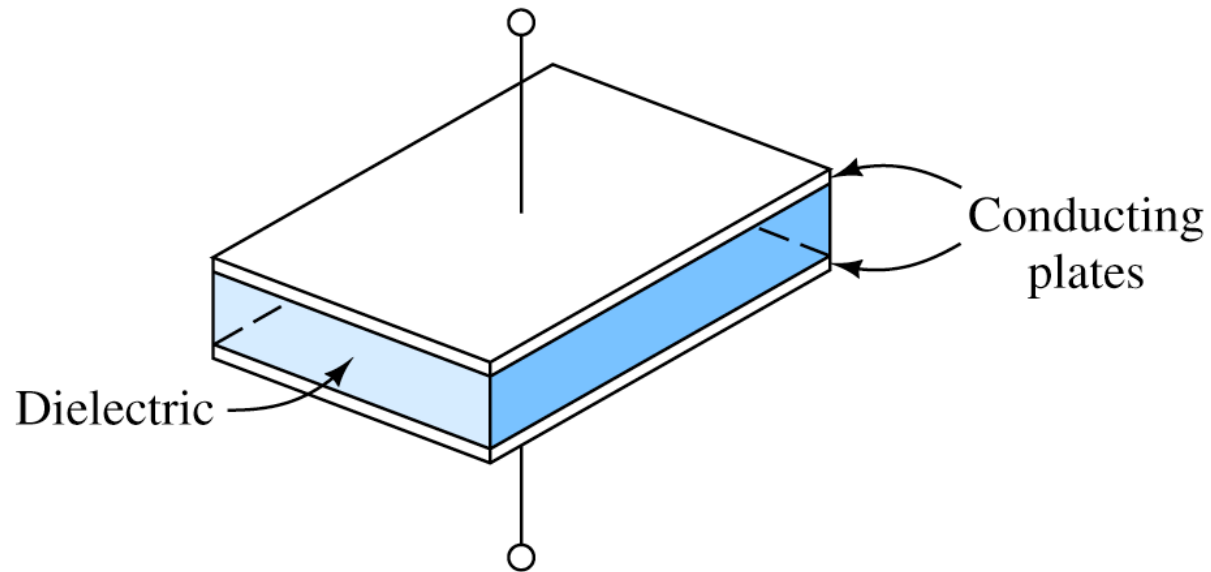

# Capacitance

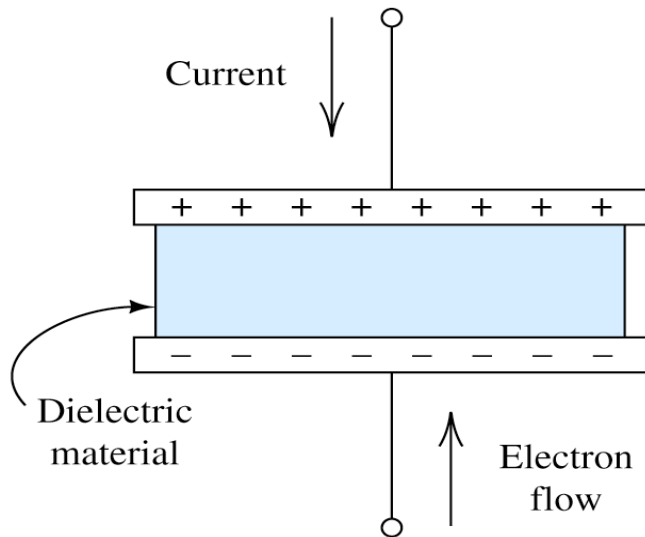

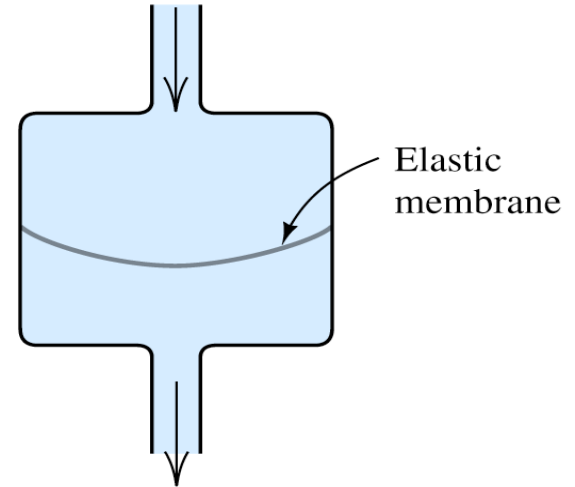(a) As current flows through a capacitor, charges of opposite sign collect on the respective plates



(b) Fluid-flow analogy for capacitance

- As charge builds up, voltage appears across capacitor
- Charge accumulated on one plate is stored in the capacitor

# Capacitance





$$q = Cv$$

$$q(t) = \int_{t_0}^t i(t)dt + q(t_0)$$





$$i = \frac{dq}{dt} = C \frac{dv}{dt}$$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(t)dt + v(t_0)$$

# Example Exercise

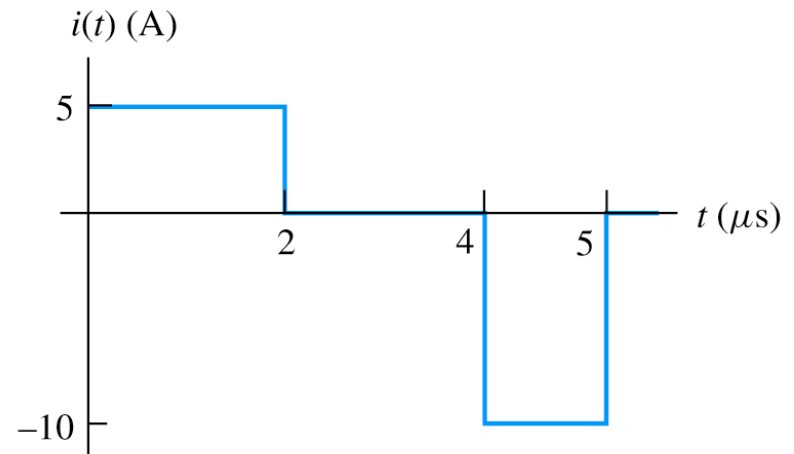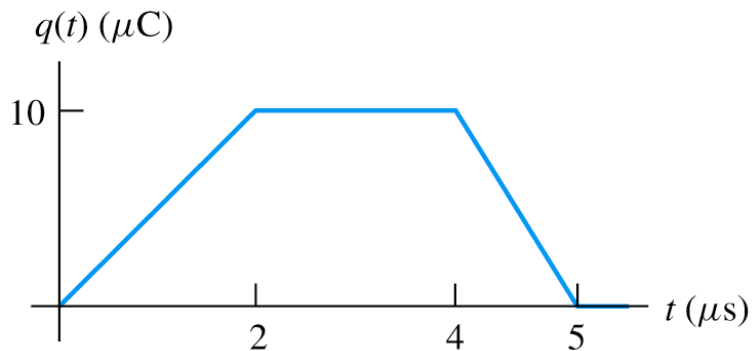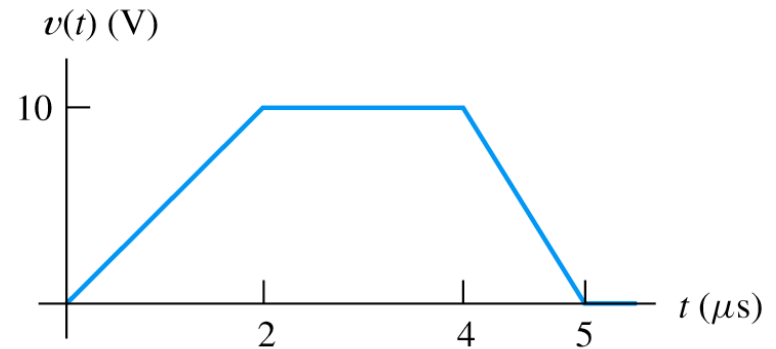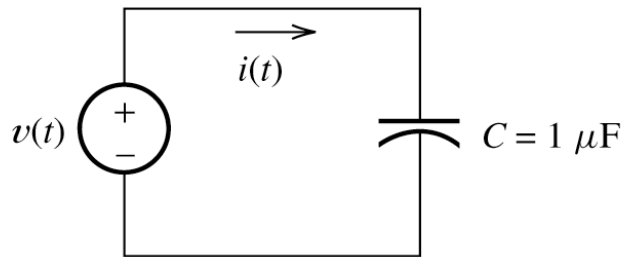

# Example Exercise

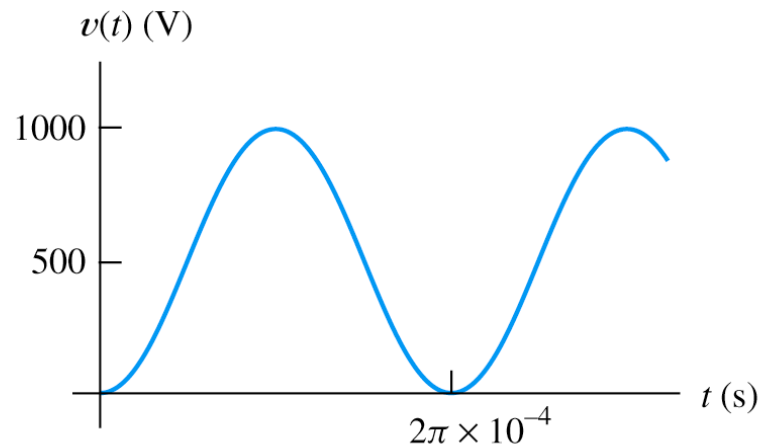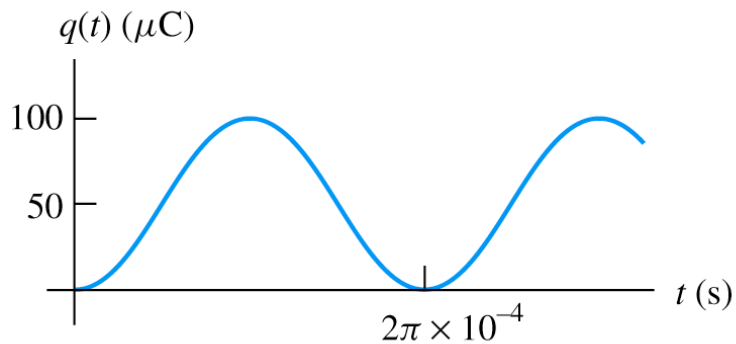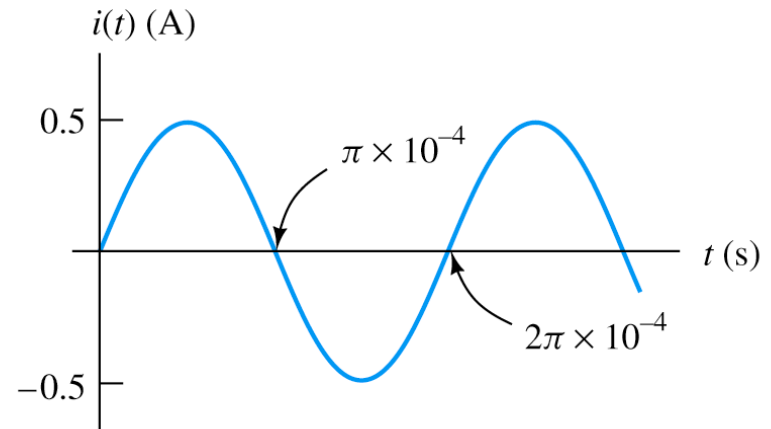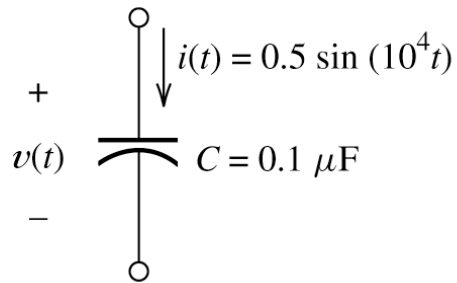

# Stored Energy and Power

$$p(t) = v(t)i(t) = Cv \frac{dv}{dt}$$





$$w(t) = \int_{t_0}^t p(t) dt = \int_{t_0}^t Cv \frac{dv}{dt} dt = \int_0^{v(t)} Cv dv = \frac{1}{2} Cv^2(t)$$

$$w(t) = \frac{1}{2} Cv^2(t) = \frac{1}{2} v(t)q(t) = \frac{q^2(t)}{2C}$$




# Example Exercise

□ 10  $\mu\text{F}$  capacitor

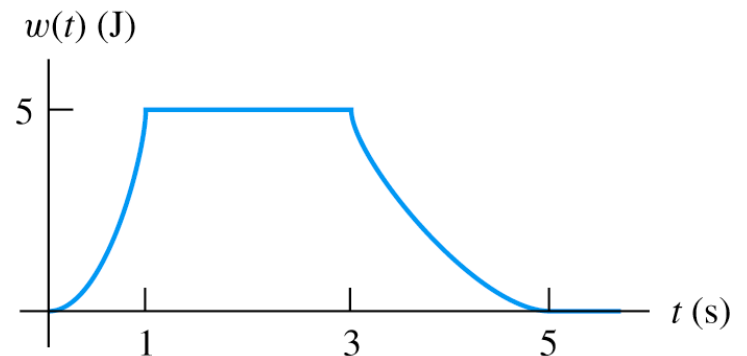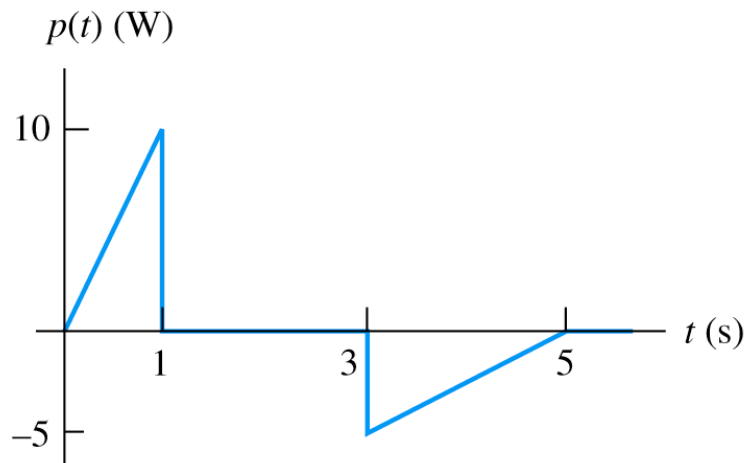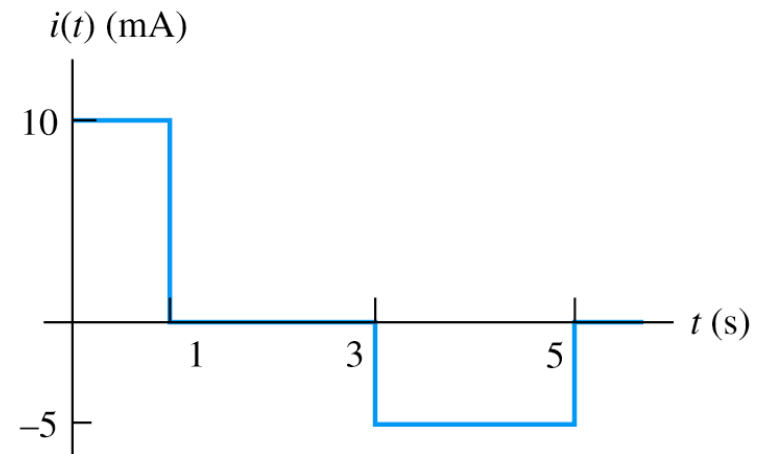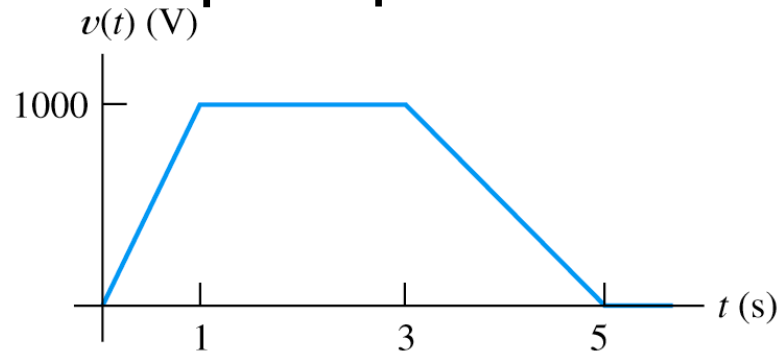


# Example Exercise


- 0.1  $\mu\text{F}$  capacitor

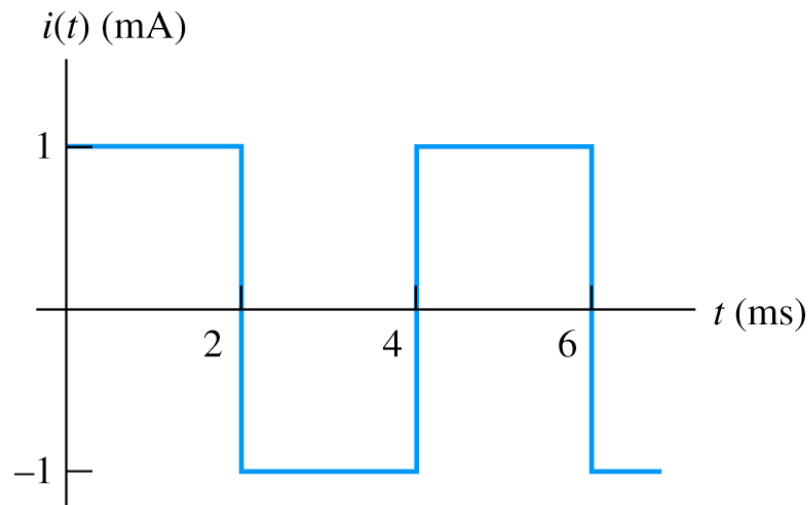


# Example Exercise (Solution)

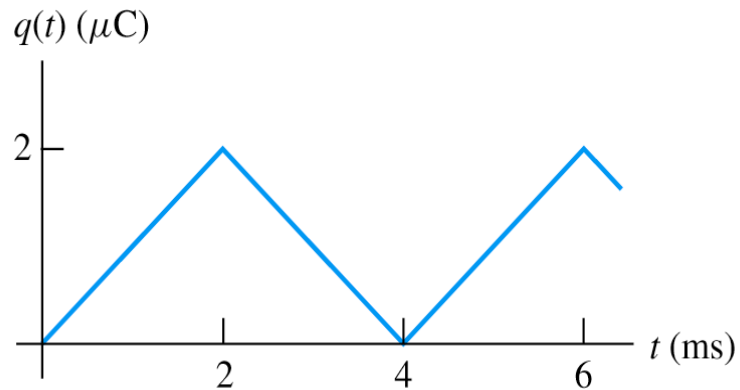


(a)

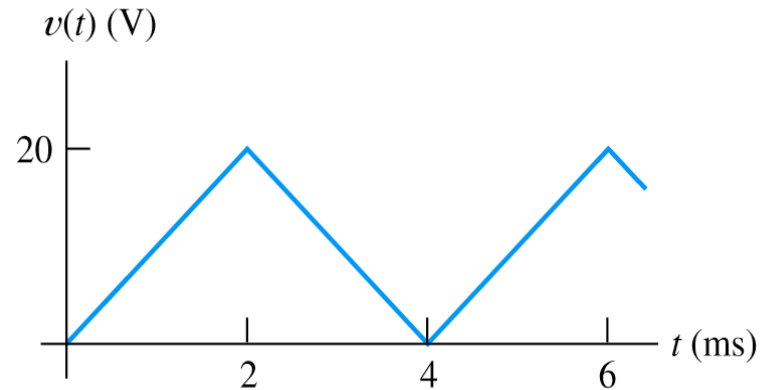

(b)

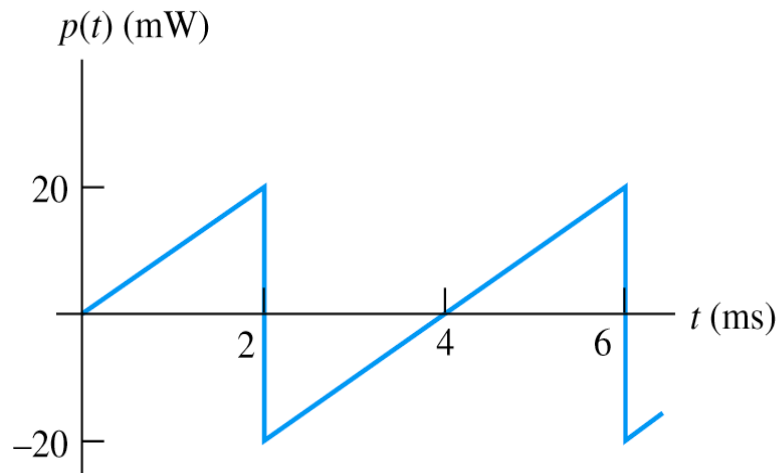


(c)

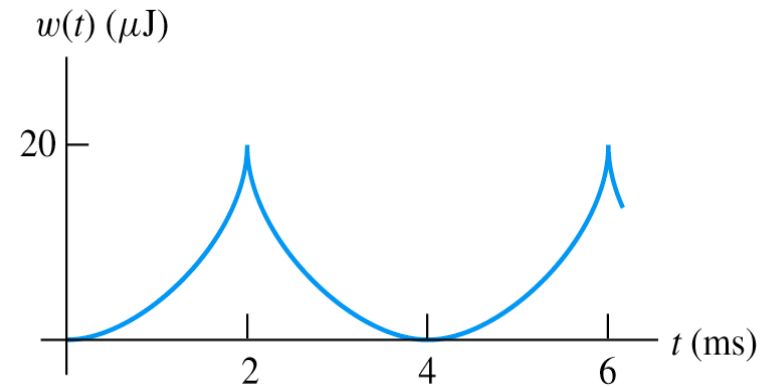

(d)

# Capacitance in Parallel

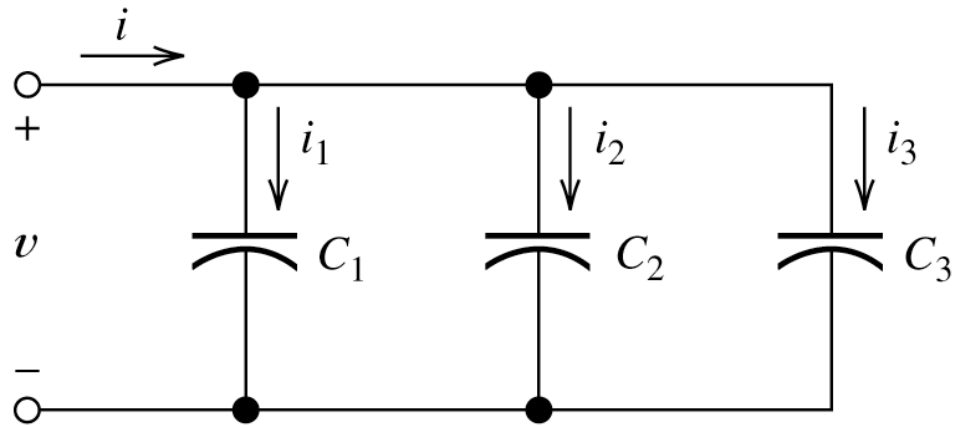


$$C_{\text{eq}} = C_1 + C_2 + C_3$$

□ Why?

□ Hint:  $i = \frac{dq}{dt} = C \frac{dv}{dt}$

# Capacitance in Series

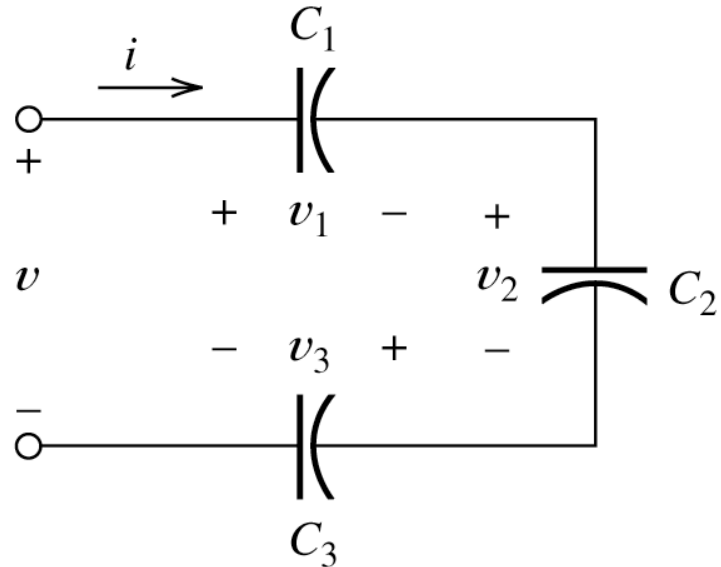


$$C_{\text{eq}} = \frac{1}{1/C_1 + 1/C_2 + 1/C_3}$$

□ Why?

# Physical Characteristics of Capacitors

- Ideal parallel plate
- Practical
  - ▣ Rolled
  - ▣ Electrolytic
  - ▣ Parasitic effects

# Parallel-Plate Capacitor

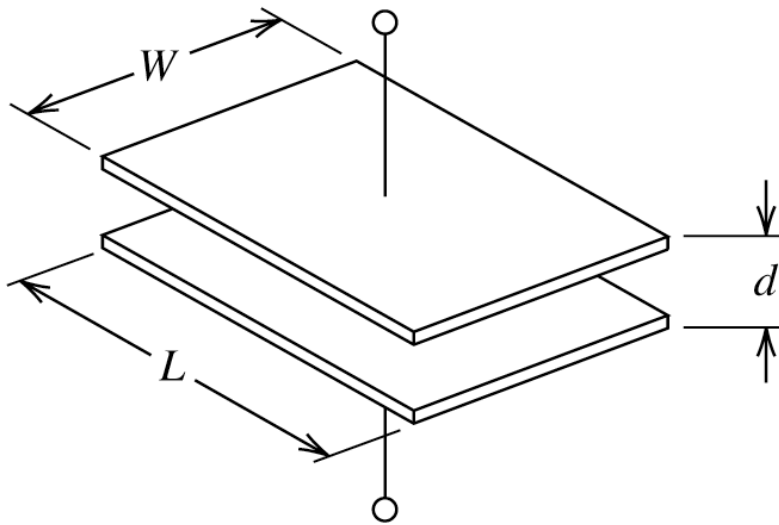

$$C = \frac{\epsilon A}{d} \quad A = WL$$

If  $d \ll W$  and  $L$

$$\epsilon_0 \cong 8.85 \times 10^{-12} \text{ F/m}$$


Dielectric constant for vacuum

$$\epsilon = \epsilon_r \epsilon_0$$

With relative dielectric constant
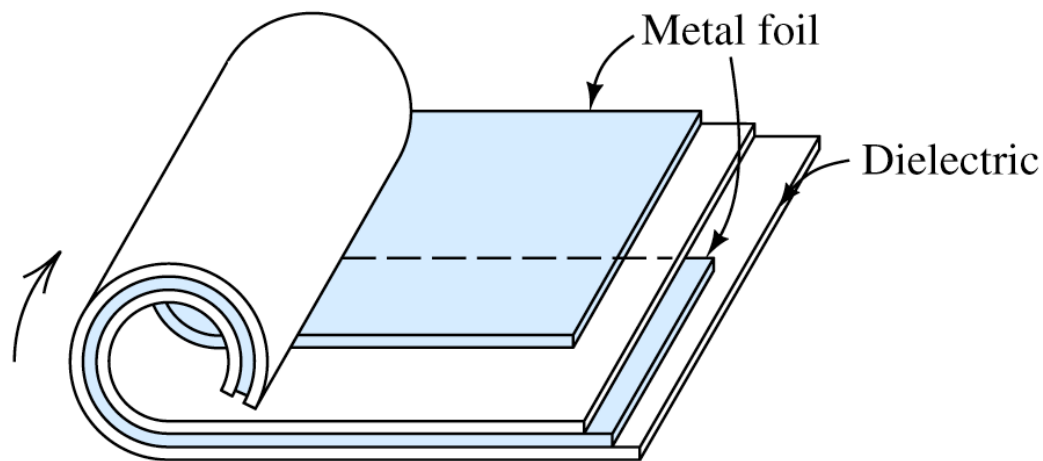
# Practical Capacitors


- Dimension too large for ideal
- Rolled up metal plates
- Dielectric materials become conductors at high electric field intensity





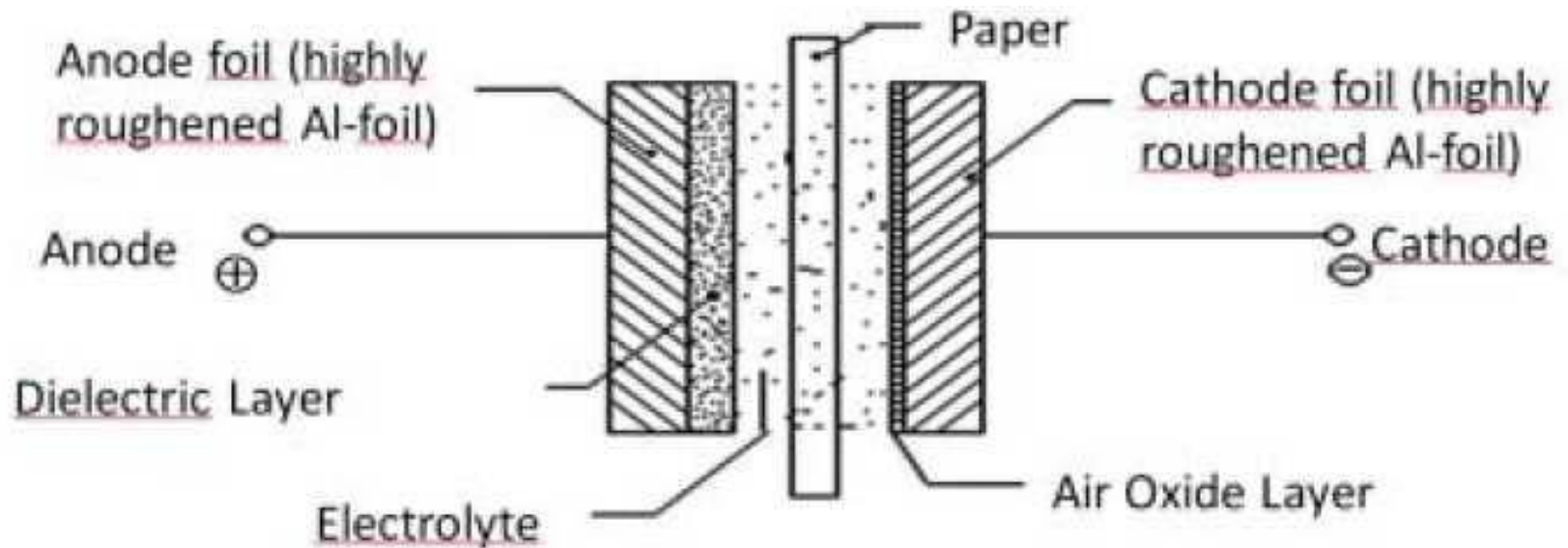
# Electrolytic Capacitors

- One plate is metallic, dielectric is oxide layer and other “plate” is electrolytic solution




# Parasitic Effects

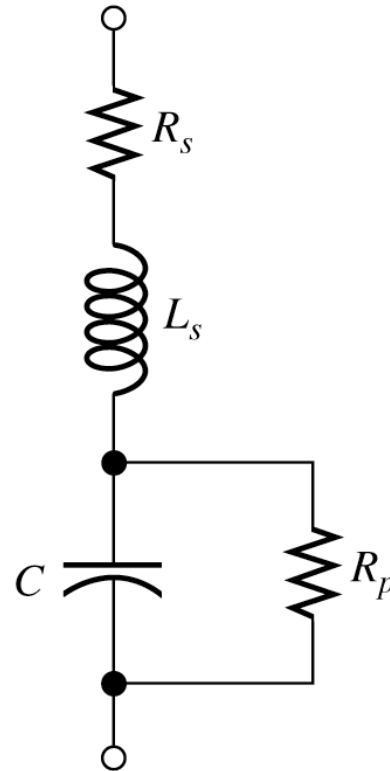
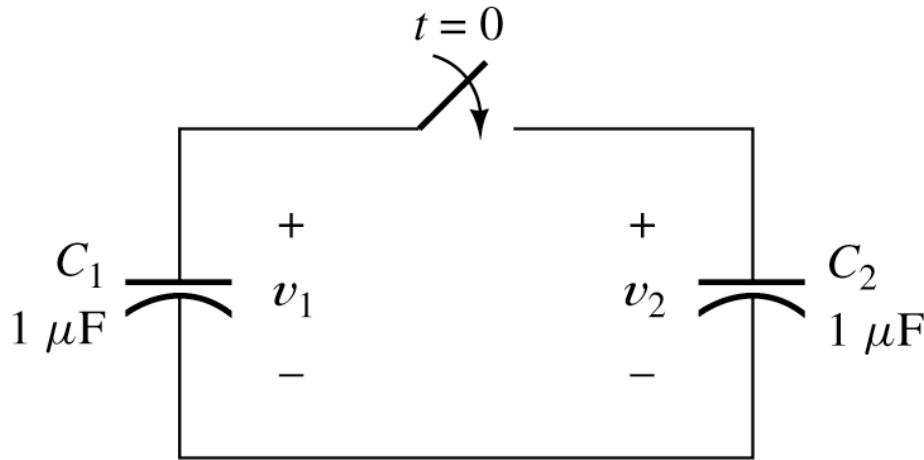
# Example Exercise


- Before  $t=0$ ,  $v_1=100\text{V}$ ,  $v_2=0\text{V}$ . Compute total energy stored before and after  $t=0$ .




- Why are they different?
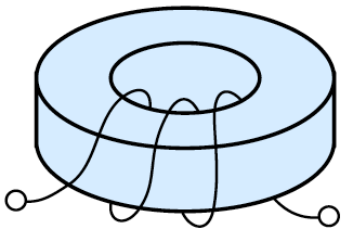
# Inductance


- Coil of wire along some form
- Current flow through coil creates flux
- Time varying flux induces voltage across coil



(a) Toroidal inductor

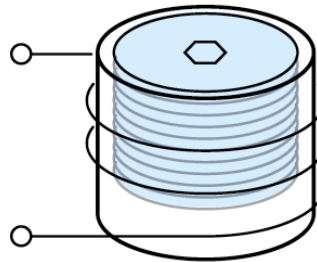

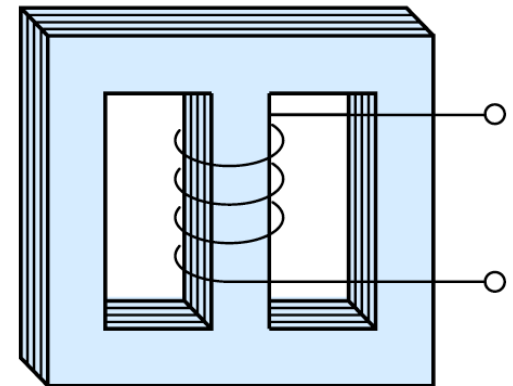(b) Coil with an iron-oxide slug that can be screwed in or out to adjust the inductance




(c) Inductor with a laminated iron core


# Inductance

- Unit of Henries (H) equivalent to volt seconds per ampere.
- As current increases, energy is stored in the magnetic field.

$$v(t) = L \frac{di}{dt}$$

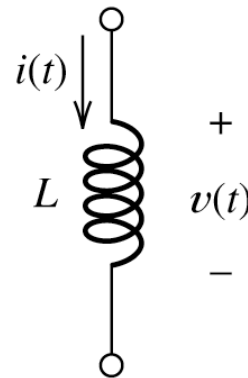

# Inductance

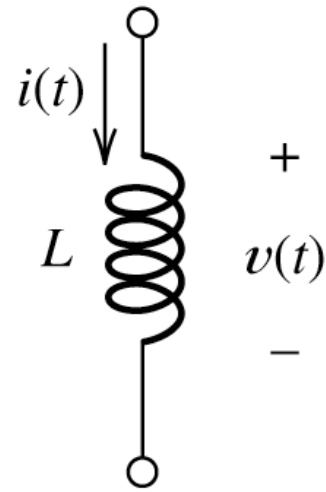

$$v(t) = L \frac{di}{dt}$$

$$v(t) = L \frac{di}{dt}$$





$$i(t) = \frac{1}{L} \int_{t_0}^t v(t) dt + i(t_0)$$

$$p(t) = Li(t) \frac{di}{dt}$$




$$w(t) = \frac{1}{2} Li^2(t)$$
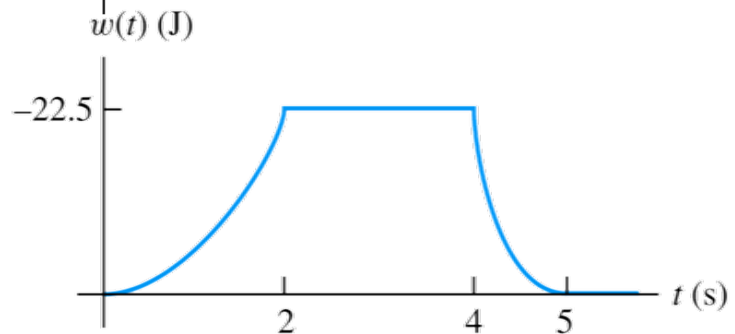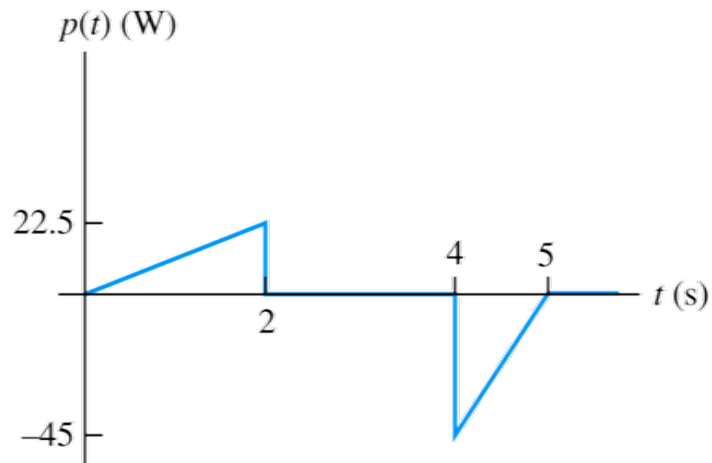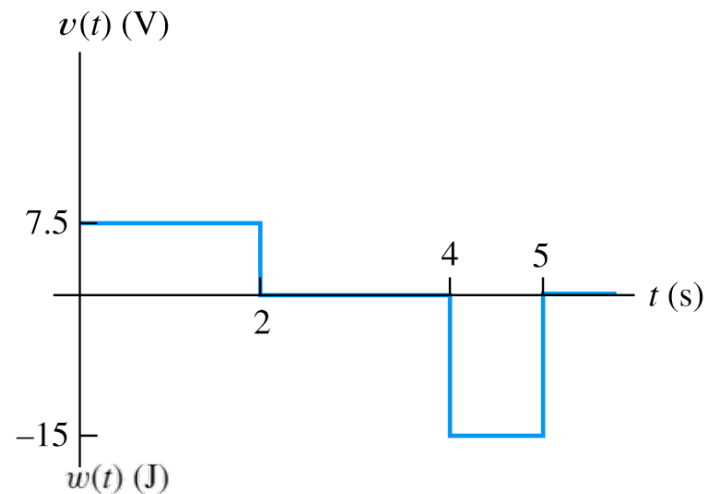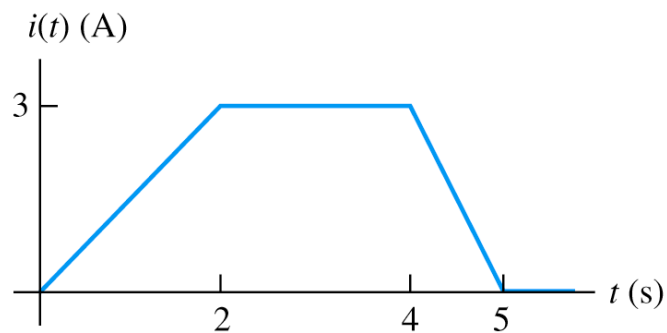
# Example Exercise

- Current through a 5 H inductor. Plot  $V$ ,  $p$ ,  $w$ .





# Example Exercise

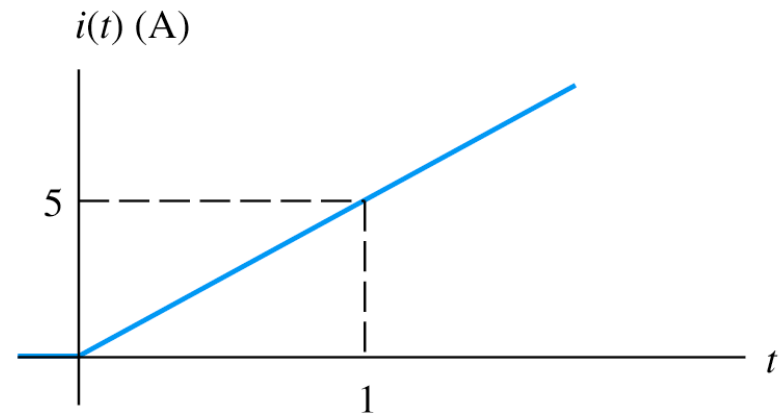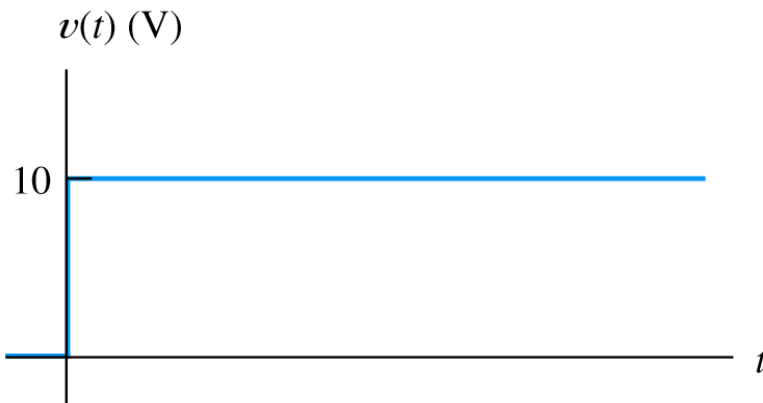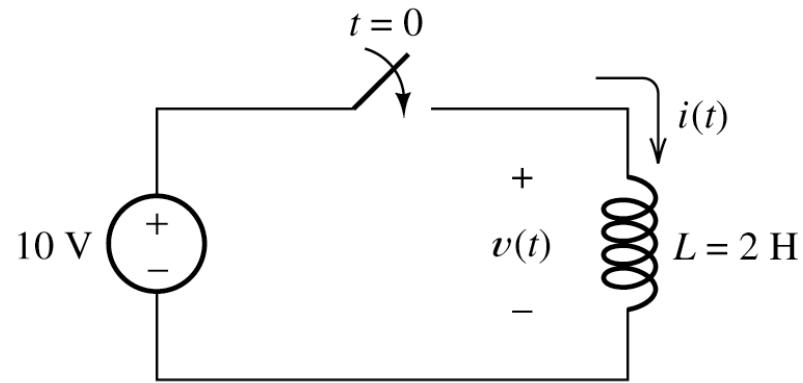



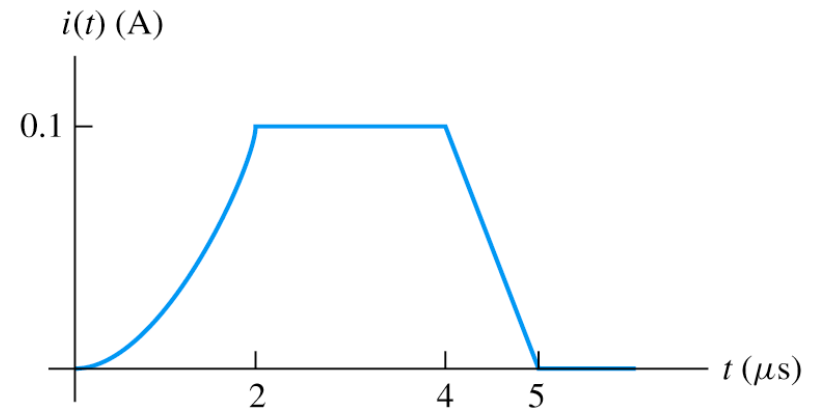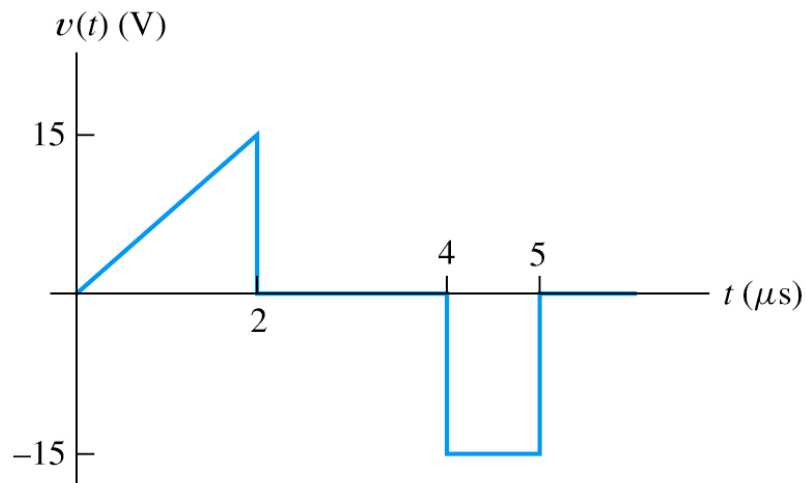
# Example Exercise

- Voltage across  $150\ \mu\text{H}$ . Plot current




# Inductance in Series

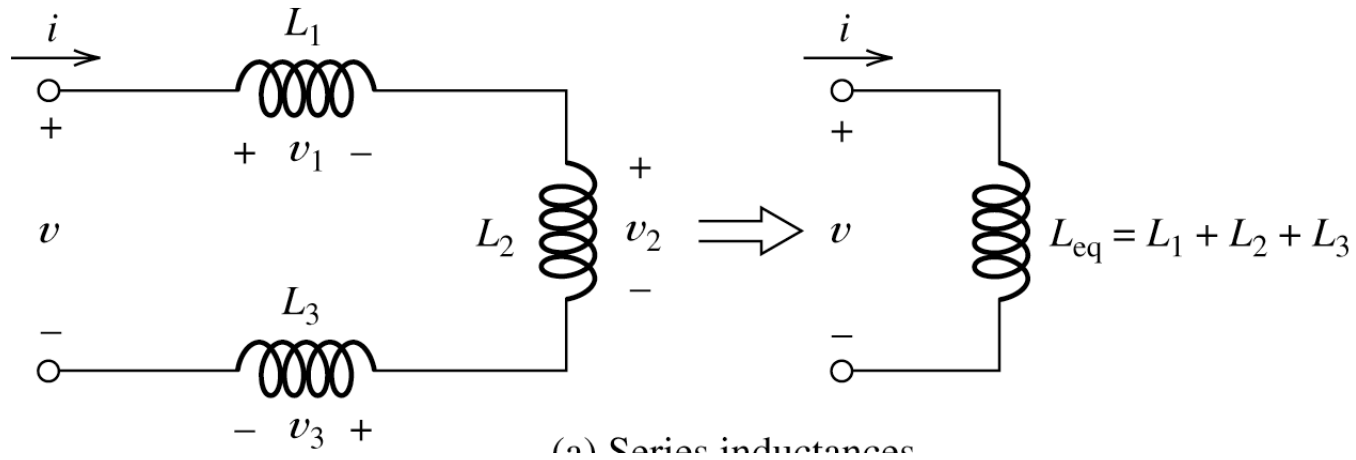



□ Why?

# Inductance in Parallel

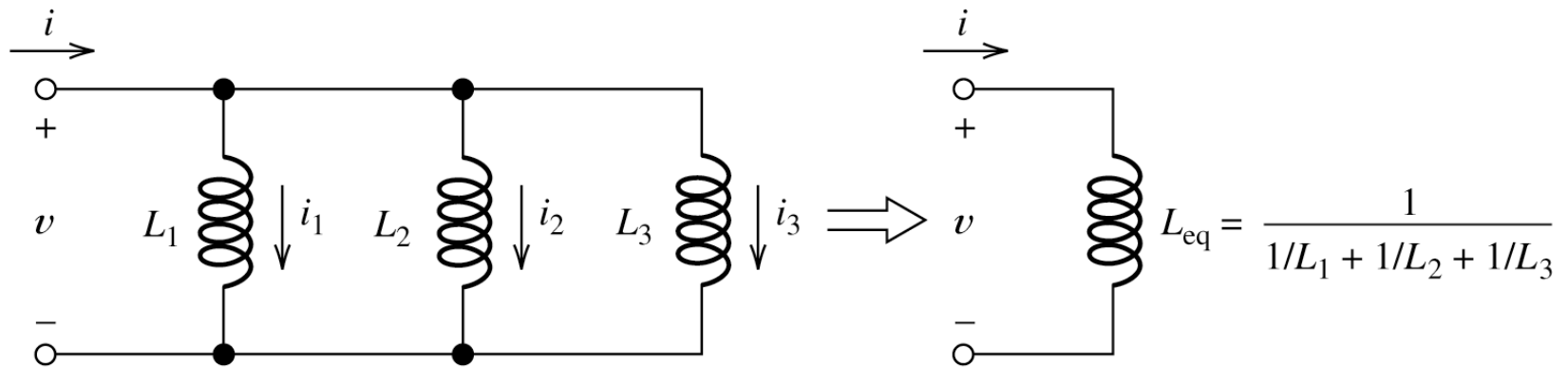


□ Why?

# Example Exercise

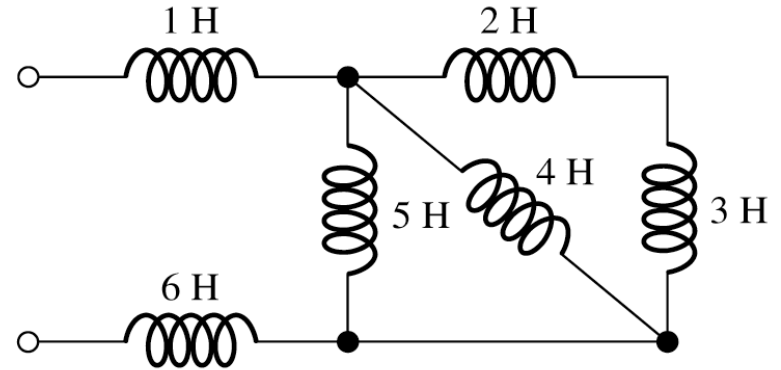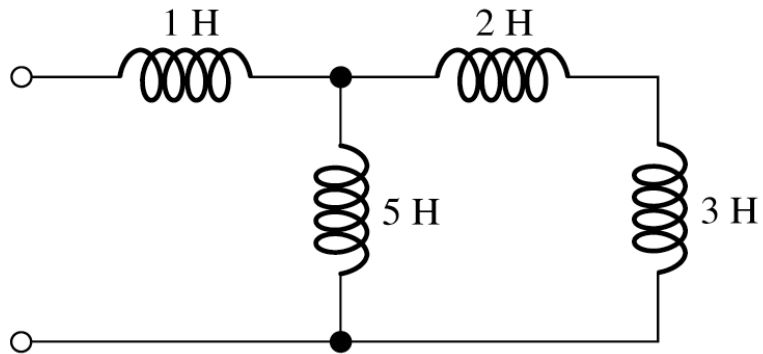


# Parasitic Effects

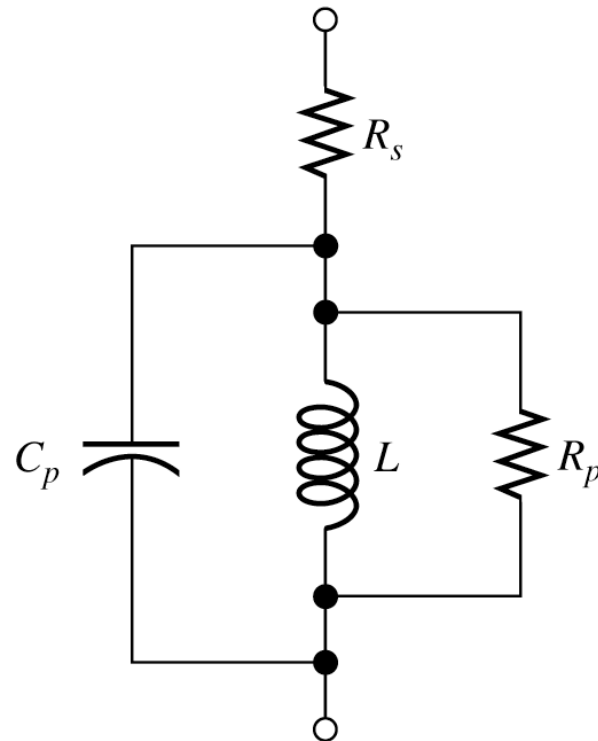

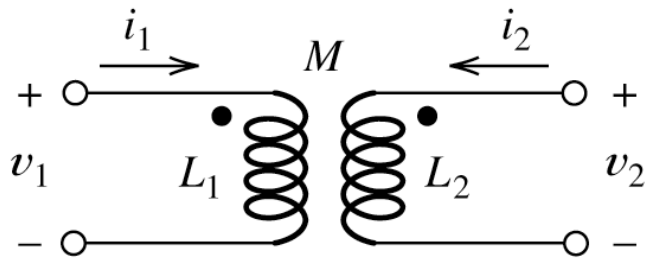
# Mutual Inductance

- Magnetic flux produced by one coil links the others (aid or oppose)



$$v_1 = L_1 \frac{di_1}{dt} + M \frac{di_2}{dt}$$
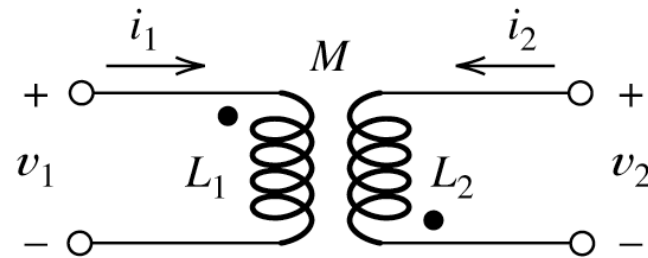
$$v_2 = M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$



$$v_1 = L_1 \frac{di_1}{dt} - M \frac{di_2}{dt}$$

$$v_2 = -M \frac{di_1}{dt} + L_2 \frac{di_2}{dt}$$

# Linear Variable Differential Transformer

- With the core centered,  $v_o(t) = 0$
- Ideally  $v_o(t) = Kx \cos(\omega t)$  where  $x$  is the displacement of the core

